

$$1. \frac{1}{C_{AB}} = \frac{1}{C_{AD}} - \frac{1}{C_{DB}} = \left(\frac{1}{C_1} - \frac{1}{C_2} \right) - \frac{1}{C_2 - C_1} = \frac{C_2 - C_1}{C_1 C_2} - \frac{1}{C_2 - C_1} = \frac{C_1^2 - 3C_1 C_2 - C_2^2}{C_1^2 C_2 - C_1 C_2^2}$$

$$C_{AB} = \frac{C_1^2 C_2 - C_1 C_2^2}{C_1^2 - 3C_1 C_2 - C_2^2} = \frac{C_2}{2} \quad \text{0,5}$$

$$\text{Alors : } C_2 C_1^2 - 3C_1 C_2^2 - C_2^3 = 2C_1^2 C_2 - 2C_1 C_2^2 = C_2^2 - C_1 C_2 - C_1^2 = 0$$

$$\text{Donc } C_2 = \frac{(-1 \pm \sqrt{5})}{2} C_1 \quad \text{0,5} \quad \text{AN : } C_2 = 5 \mu F \quad \text{0,5}$$

2. Tension et charge aux bornes de chaque condensateur.

$$C_{AB} = \frac{Q_{AB}}{U_{AB}} = \frac{C_2}{2} = Q_{AB} = \frac{C_2 U_{AB}}{2} \quad \text{AN } Q_{AB} = 1.25 \text{ mC} \quad \text{0,5}$$

$$\text{Comme } Q_{AB} = Q_{AD} = Q_{DB} = 1.25 \text{ mC} = Q_{1AD} = Q_{2AD} = 1.25 \text{ mC}$$

$$U_{1AD} = \frac{Q_{1AD}}{C_1} = 156 \text{ V} \quad \text{0,25}$$

$$\text{Et } U_{2AD} = \frac{Q_{2AD}}{C_2} = 250 \text{ V} \quad \text{0,25}$$

$$U_{DB} = U_{AB} - U_{1AD} - U_{2AD} = 94 \text{ V} \quad \text{0,25}$$

$$Q_{1DB} = U_{DB} C_1 = 0.752 \text{ mC} \quad \text{0,25}$$

Et

$$Q_{2DB} = U_{DB} C_2 = 0.47 \text{ mC} \quad \text{0,25}$$


Exercice 4 :

1. Valeur de X :

$$\frac{1}{C_{eq}} = \frac{1}{C} + \frac{1}{C+X} = \frac{1}{X} \Rightarrow \textcircled{0,5}$$

$$X^2 + CX - C^2 = 0 \Rightarrow$$
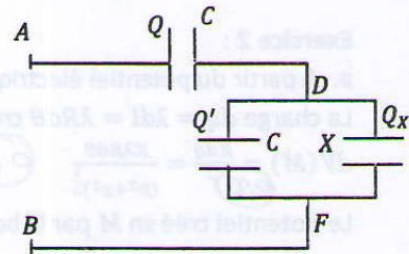
$$X = \frac{-C + \sqrt{5}C}{2} \Rightarrow X = 1.85 \mu F \quad \textcircled{0,5}$$



2. Charges et tensions.

On a $Q = Q_{eq}$ et $Q_{eq} = C_{eq}V = XV = 7.4 \cdot 10^{-4} C$ donc $Q = 7.4 \cdot 10^{-4} C$ $\textcircled{0,5}$

On a $V_A - V_D = \frac{Q}{C} = \frac{Q_{eq}}{C} = \frac{X}{C}V \Rightarrow V_A - V_D = 247 V$ $\textcircled{0,5}$

$V_D - V_F = V - (V_A - V_D) \Rightarrow V_D - V_F = 153 V$ $\textcircled{0,5}$

$Q' = C(V_D - V_F) \Rightarrow Q' = 4.6 \cdot 10^{-4} C$ $\textcircled{0,1}$

$Q_X = X(V_D - V_F) \Rightarrow Q_X = 2.8 \cdot 10^{-4} C$ $\textcircled{0,1}$

Exercice 5 :

1. $\frac{1}{R_{eq}} = \frac{1}{R_1 + R_2} + \frac{1}{R_3}$ $\textcircled{0,5}$ $R_{eq} = 50 \Omega$


$e = R_{eq}I$, $\textcircled{1}$ $I = \frac{e}{R_{eq}} = 1 A$

2. $V_A - V_B = e = 50V$. $\textcircled{0,5}$

Exercice 3

Nœuds:

$$I_1 + I_2 = I_3 \quad (1)$$

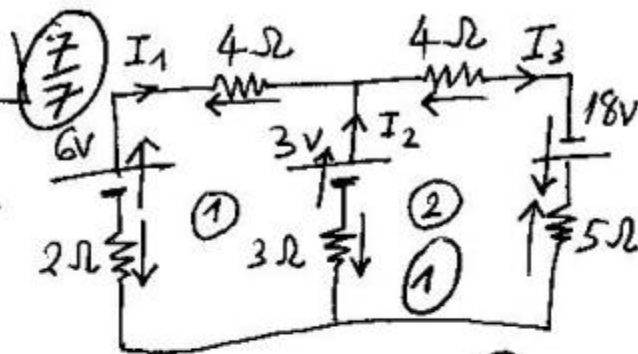

Mailles: (1) $6 + 3I_2 = 4I_1 + 3 + 2I_1$ (1)

(2) $3 + 18 = 3I_2 + 4I_3 + 5I_3$ (1)

$$\begin{cases} 6I_1 - 3I_2 = 3 \\ 9I_1 + 12I_2 = 21 \end{cases} \Rightarrow \begin{cases} 2I_1 - I_2 = 1 \\ 3I_1 + 4I_2 = 7 \end{cases}$$

Tout calcul fait, on obtient:

$$I_1 = 1A, \quad I_2 = 1A, \quad I_3 = 2A$$

Le du Module