


Practice 5: CMOS Inverter

Exercise 1

The following CMOS inverter has these parameters:

$$V_{Tn} = 1V \quad V_{Tp} = -1.5V \quad k_n = 100 \frac{\mu A}{V^2} \quad k_p = 50 \frac{\mu A}{V^2}$$

 Find Nominal Voltage Levels and draw the VTC.



Solution:

1. We'll start with $V_{in}=0$. In this case, N1 is cut-off and there is no path to ground, so after filling up an output capacitance to V_{DD} , there are no static currents. $V_{OHmax}=V_{DD}$.
2. As we raise V_{in} , N1 stays in cut-off until $V_{in}=V_{GS}>V_T$. On the other hand, P1 is open ($V_{SG} \rightarrow V_{DD}$) with a low voltage across its output ($V_{SD} \rightarrow 0$), meaning we are in the linear region.

$$I_{Dp} = k_p \left[(V_{SGp} - |V_{Tp}|) V_{SDp} - \frac{V_{SDp}^2}{2} \right]$$

3. Once $V_{in}>V_{Tn}$, N1 starts conducting in the saturation region. To find V_{OHmin} and V_{IL} , we will first equate the two currents and then look for the point where gain=-1 by differentiating:

$$I_{Dp} = k_p \left[(V_{SGp} - |V_{Tp}|) V_{SDp} - \frac{V_{SDp}^2}{2} \right] = k_p \left[(V_{DD} - V_{in} - |V_{Tp}|)(V_{DD} - V_{out}) - \frac{(V_{DD} - V_{out})^2}{2} \right]$$

$$I_{Dn} = \frac{k_n}{2} (V_{GSn} - V_{Tn})^2 (1 + \lambda V_{DS}) \approx \frac{k_n}{2} (V_{in} - V_{Tn})^2$$

$$I_{Dp} = I_{Dn} = 50 \left[(3.5 - V_{in})(5 - V_{out}) - \frac{(5 - V_{out})^2}{2} \right] = 50(V_{in} - 1)^2$$

$$5 - 5V_{in} + 1.5V_{out} + V_{in}V_{out} - 0.5V_{out}^2 = V_{in}^2 - 2V_{in} + 1$$

We'll differentiate both sides by dV_{in} :

$$-5 + 1.5 \frac{dV_{out}}{dV_{in}} + V_{out} + V_{in} \frac{dV_{out}}{dV_{in}} - V_{out} \frac{dV_{out}}{dV_{in}} = 2V_{in} - 2$$

$$\text{Now we'll substitute } \frac{dV_{out}}{dV_{in}} = -1 \text{ and get: } V_{in} = \frac{2V_{out} - 4.5}{3}$$

We'll put V_{in} back in the original equation and get:

$$5 - 5 \frac{2V_{out} - 4.5}{3} + 1.5V_{out} + \frac{2V_{out} - 4.5}{3} V_{out} - 0.5V_{out}^2 = \left(\frac{2V_{out} - 4.5}{3} - 1 \right)^2$$

$$12.5 - \frac{10}{3}V_{out} + \frac{1}{6}V_{out}^2 = \frac{4}{9}V_{out}^2 - \frac{10}{3}V_{out} + 6.25$$

$$V_{out}^2 = 22.5 \quad V_{OHmin} = 4.7V \quad V_{IL} = 1.66V$$

In the same fashion, we'll find V_{OLmax} and V_{IH} , though this time, P1 is saturated and N1 is linear:

$$I_{Dn} = k_n \left[(V_{GSn} - V_{Tn})V_{DSn} - \frac{V_{DSn}^2}{2} \right] = k_n \left[(V_{in} - V_{Tn})V_{out} - \frac{V_{out}^2}{2} \right]$$

$$I_{Dp} = \frac{k_p}{2} (V_{SGp} - |V_{Tp}|)^2 (1 + \lambda V_{SDp}) \approx \frac{k_p}{2} (V_{DD} - V_{in} - |V_{Tp}|)^2$$

$$I_{Dn} = I_{Dp} = 100 \left[(V_{in} - 1)V_{out} - \frac{V_{out}^2}{2} \right] = 25(5 - V_{in} - 1.5)^2$$

$$4(V_{in}V_{out} - V_{out} - 0.5V_{out}^2) = 12.25 - 7V_{in} + V_{in}^2$$

Differentiating and substituting $\frac{dV_{out}}{dV_{in}} = -1$ gives us:


$$4 \left(V_{out} + V_{in} \frac{dV_{out}}{dV_{in}} - \frac{dV_{out}}{dV_{in}} - V_{out} \frac{dV_{out}}{dV_{in}} \right) = 2V_{in} - 7 \quad V_{in} = \frac{8V_{out} + 11}{6}$$

Substituting into the original equation:

$$4 \left(\frac{8V_{out} + 11}{6} V_{out} - V_{out} - 0.5V_{out}^2 \right) = \left(3.5 - \frac{8V_{out} + 11}{6} \right)^2$$

$$\frac{14}{9} V_{out}^2 + \frac{70}{9} V_{out} - \frac{25}{9} = 0 \quad V_{OLmax} = 0.33 \quad V_{IH} = 2.27$$

4. Finally, when $V_{in}=5V$, P1 is cut-off and there is no path to V_{DD} , so after discharging the output capacitance, there are no static currents. $V_{OLmin}=0V$
5. We can now draw the VTC:

 

Exercise 2: Propagation Delay

Given an inverter with the following properties:

$$\frac{(W/L)_p}{(W/L)_n} = 3.4 \quad L_{min} = 0.25 \mu m \quad (W/L)_{min} = 1.5 \quad (\text{Assume long channel})$$

fabricated in an $0.25 \mu m$ process with the following process characteristics:

$V_{DD}=2.5V$	$V_{T0}[V]$	$\gamma[\sqrt{V}]$	$k'[\frac{\mu A}{V^2}]$	$\lambda[V^{-1}]$
nMOS	0.43	0.4	115	0.06
pMOS	-0.4	-0.4	-30	-0.1

Derive the High to Low propagation delay (t_{pHL}) driving a $50fF$ capacitance.