

People's Democratic Republic of Algeria
Ministry of Higher Education and Scientific Research
Mohamed Boudiaf University of M'sila
Faculty of Sciences

Common Trunk of Matter Sciences

Practical works - Physics 2

1st year - 2nd semester

5th Practical Work

Transformer

Experiment date:/...../.....

Corrector professor :

Report prepared by :

| First name | Family name | Group | Sup-group | Preparation mark | Final mark |
|-------------------|--------------------|--------------|------------------|-------------------------|-------------------|
| | | | | /5,00 | /20,00 |
| | | | | /5,00 | /20,00 |
| | | | | /5,00 | /20,00 |
| | | | | /5,00 | /20,00 |
| | | | | /5,00 | /20,00 |
| | | | | /5,00 | /20,00 |
| | | | | /5,00 | /20,00 |

Academic year : 2023/2024

1-Purpose of the experiment

The aim of this experience is to highlight the transformation by raising or lowering tensions.

2-Notions and preparation

In Figure -1- a transformer is schematically represented. The parameters on the left side are those of the primary, while those on the right represent the secondary. By applying a sinusoidal voltage to the primary circuit consisting of a winding of “ n_1 ” turns, what happens on the secondary of “ n_2 ” turns?

Let the primary voltage be $U_1 = U_0 \sin(\omega t + \theta)$. The current passes through the primary winding around the ferromagnet, it will create a magnetic flux Φ in the iron which will in turn induce an electromotive force “e.m.f. »given by the relation:

$$E_{in} = -n_1 \frac{d\Phi}{dt}$$

For an ideal transformer, the primary voltage U_1 is equal to the “e.m.f. » induced.

$$E_{in} = -U_1 = -U_0 \sin(\omega t + \theta)$$

For reasons of high efficiency, the iron is made up of a stack of varnished sheets.

Under these conditions the flow Φ is completely channeled in the iron and will be recovered in the secondary, where it will create an e.m.f. which in the case of a no-load transformer, will be equal to the voltage which will be delivered by the secondary winding.

$$U_2 = V_0 \sin(\omega t + \beta)$$

Moreover

$$U_2 = n_2 \frac{d\Phi}{dt}$$

1- Since the flow is conserved. Find the following relationship:

$$\frac{U_1}{n_1} = \frac{U_2}{n_2}$$

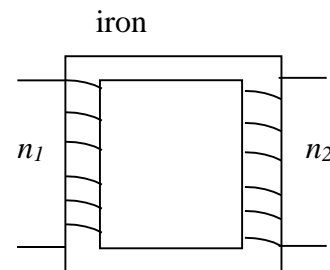


Figure-1

.....

Therefore we find the expression of the output voltage (that of the secondary) given by:

$$U_2 = \frac{n_2}{n_1} U_1 = m U_1$$

“ m ” is the turns transformation ratio.

2- What is the condition on m for the transformer to be step-up? m

3- What is the condition on m for the transformer to be step-down? m

4- What is a diode?

.....

3-Practical work

3-1-Perform the experimental setup in figure -2-.

-Power the circuit with a voltage $V= 5.0V$, so that it is constant throughout the experiment.

-For a fixed primary winding of $n_1 = 300$ turns, note the secondary voltage.

| | | | | | |
|-------------------|----|----|----|-----|-----|
| n_2 (turns) | 14 | 42 | 84 | 112 | 140 |
| U_2 (Volts) | | | | | |
| $\frac{U_2}{U_1}$ | | | | | |
| $\frac{n_2}{n_1}$ | | | | | |

1°- Complete the above table.

2°- Compare the voltage ratios and those of the windings.

.....

3°- Comment.

.....

3-2 A- Take a fixed primary winding $n_1 = 300$ turns.

-Take a fixed secondary winding $n_2 = 42$ turns.

-Read the secondary voltage, $U_2 = \dots V$; give the value of " $m = \dots$ "

B- Now reverse the windings so that the primary becomes the secondary.

-Read the secondary voltage, $U_2 = \dots V$; give the value of " $m = \dots$ "

-What do you see in both cases (A and B)?

.....

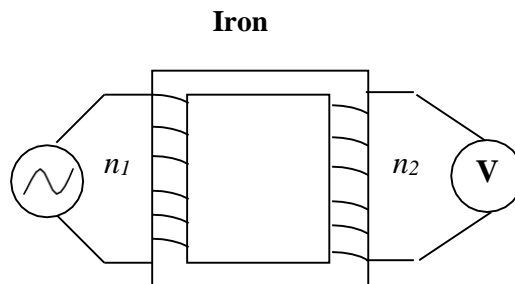


Figure-2


3-3 To transform the output AC signal into a DC signal, a rectifier is mounted at the output of the

transformer, as shown in figure-3.

-Take a fixed primary winding $n_1 = 300$ turns.

-Take a fixed secondary winding $n_2 = 42$ turns.

Using an oscilloscope to view the signals at the transformer output (CH1) and the rectifier output (CH2).

Note:  is the electronic symbol for diode.



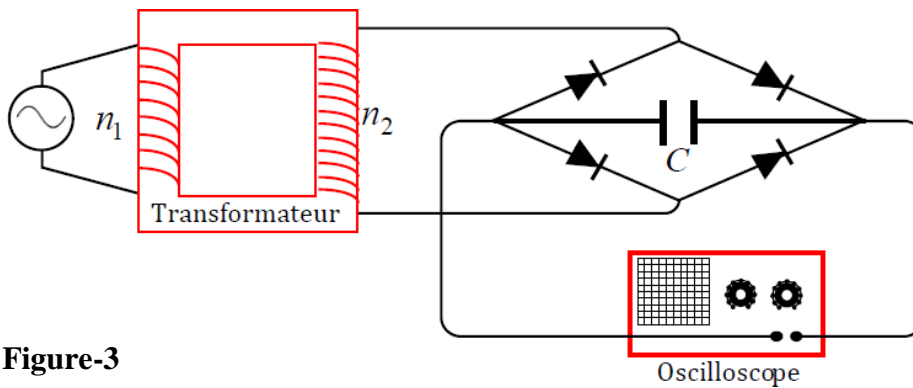


Figure-3

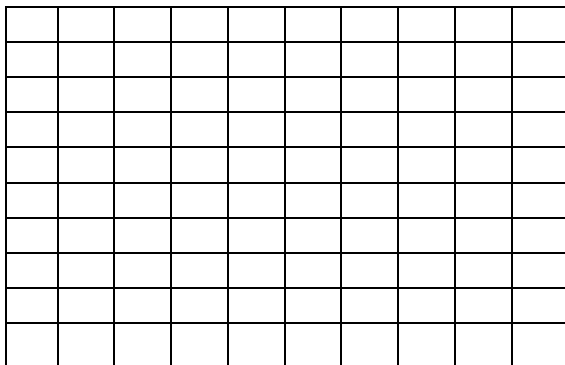

The voltage U_2 ; before rectifying

| | |
|---|---|
| $S_h = \dots \dots \dots \text{ms/div}$ | $S_v = \dots \dots \dots \text{ms/div}$ |
|---|---|

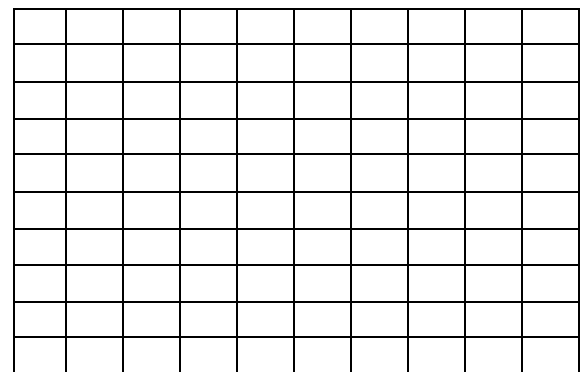

The voltage U_2 ; after rectifying

| | |
|---|---|
| $S_h = \dots \dots \dots \text{ms/div}$ | $S_v = \dots \dots \dots \text{ms/div}$ |
|---|---|

4-Conclusion:

.....

.....

.....

.....

.....

.....