

Physics 02: Electricity and magnetism

University Year 2023-2024

Series N° 03: ELECTROKINETICS

EXERCISE 01

- The radius of the cable (r).

$$\text{We have: } V = R \cdot I \Rightarrow R = \frac{V}{I} = \frac{1.6 \times 10^{-2}}{1200} \Rightarrow R = 1.33 \times 10^{-5} \Omega \text{ (R: resistance)}$$

$$R = \rho \frac{L}{S} \Rightarrow S = \frac{\rho L}{R} \Rightarrow S = \frac{1.72 \times 10^{-8} \times 0.24}{1.33 \times 10^{-5}} \Rightarrow S = 3.1 \times 10^{-4} \text{ m}^2 \text{ (S: surface)}$$


The cable has a circular cross-section, so that:

$$S = \pi r^2$$

$$\Rightarrow r = \sqrt{\frac{S}{\pi}} = \sqrt{\frac{3.1 \times 10^{-4}}{\pi}} \Rightarrow r = 9.93 \times 10^{-3} \text{ m} = 9.93 \text{ mm}$$

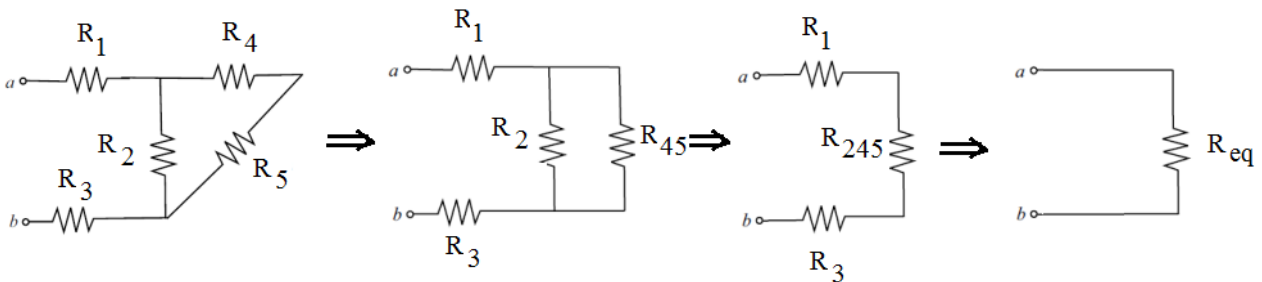EXERCISE 02

The equivalent resistance between points a and b.




$$R_4 \text{ and } R_5 \text{ are in series: } R_{45} = R_4 + R_5 = 5.1 + 3.5 \Rightarrow R_{45} = 8.6 \Omega$$

$$R_{45} \text{ and } R_2 \text{ are in parallel: } \frac{1}{R_{245}} = \frac{1}{R_{45}} + \frac{1}{R_2} = \frac{1}{8.6} + \frac{1}{1.8} \Rightarrow R_{245} = 1.5 \Omega$$

$$R_1, R_{245} \text{ and } R_3 \text{ are in series: } R_{eq} = R_1 + R_{245} + R_3 = 2.4 + 1.5 + 3.6 \Rightarrow R_{eq} = 7.5 \Omega$$

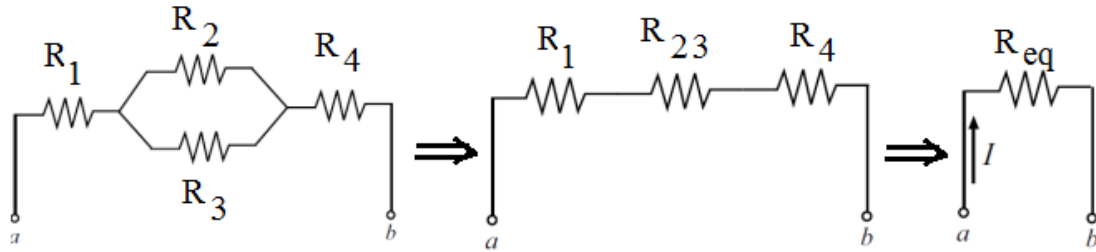EXERCISE 03

1- The equivalent resistance between points a and b



R_2 and R_3 are in parallel: $\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{7} + \frac{1}{10} \Rightarrow R_{23} = 4.12 \Omega$

R_1 , R_{23} and R_4 are in series: $R_{eq} = R_1 + R_{23} + R_4 = 4 + 4.12 + 9 \Rightarrow R_{eq} = 17.12 \Omega$

2- The current in each resistor if a potential difference of 34.0V is applied between points a and b

$$V_{ab} = R_{eq}I \Rightarrow I = \frac{V_{ab}}{R_{eq}} = \frac{34}{17.12} \Rightarrow I = 1.99 A$$

R_1 , R_{23} and R_4 are in series: $I = I_1 = I_{23} = I_4 = 1.99 A$

$$V_{ab} = V_1 + V_{23} + V_4$$

$$V_1 = R_1 \cdot I_1 = 4 \times 1.99 = 7.96 V$$

$$V_4 = R_4 \cdot I_4 = 9 \times 1.99 = 17.90 V$$

\Rightarrow

$$V_{23} = V_{ab} - (V_1 + V_4) = 34 - (7.96 + 17.9) = 8.1 V$$

$$V_{23} = V_2 = V_3 = 8.1 V$$

$$V_2 = R_2 \cdot I_2 \Rightarrow I_2 = \frac{V_2}{R_2} = \frac{8.1}{7} \Rightarrow I_2 = 1.16 A$$

$$V_3 = R_3 \cdot I_3 \Rightarrow I_3 = \frac{V_3}{R_3} = \frac{8.1}{10} \Rightarrow I_3 = 0.81 A$$

EXERCISE 04

The currents I_1 , I_2 and I_3 .

According to **Kirchhoff's Current Law**:

$$I_1 + I_2 = I_3 \dots \dots \dots \text{eq.1}$$


According to **Kirchhoff's Voltage Law**:

From loop 1:

$$12 V = 4 I_3 + 1 I_1 \dots \dots \dots \text{eq.2}$$

From loop 2:
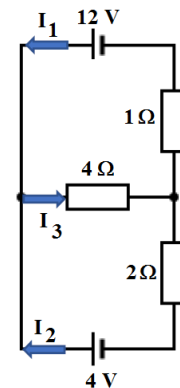
$$4 V = 4 I_3 + 2 I_2 \dots \dots \dots \text{eq.3}$$



$$\text{eq.2} \Rightarrow I_1 = 12 - 4 I_3$$

$$\text{eq.3} \Rightarrow I_2 = \frac{4 - 4 I_3}{2} \Rightarrow I_2 = 2 - 2 I_3$$

$$I_1 + I_2 = I_3$$

$$\Rightarrow 12 - 4 I_3 + 2 - 2 I_3 = I_3$$

$$\Rightarrow 14 = 7 I_3$$


$$\Rightarrow I_3 = 2 \text{ A}$$

$$I_1 = 12 - 4 I_3 = 12 - 4 \times 2 \Rightarrow I_1 = 4 \text{ A}$$

$$I_2 = 2 - 2 I_3 = 2 - 2 \times 2 \Rightarrow I_2 = -2 \text{ A}$$

I_2 is in the opposite chosen direction

$$I_1 = I_2 + I_3$$

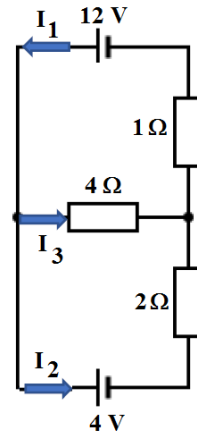

EXERCISE 05

The current flowing in the network.

We assume that the directions of currents are as follow:

According to Kirchhoff's Current Law:

$$I_1 = I_2 + I_3 \dots \dots \dots \text{eq.1}$$


According to Kirchhoff's Voltage Law:

From loop 1:

$$20 \text{ V} = 6 I_2 + 10 I_2 + 3 I_1 \dots \dots \dots \text{eq.2}$$

From loop 2:
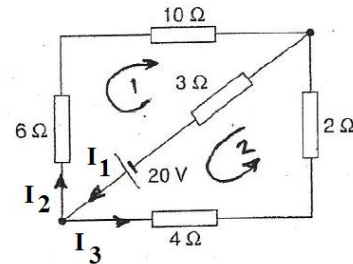
$$20 \text{ V} = 4 I_3 + 2 I_3 + 3 I_1 \dots \dots \dots \text{eq.3}$$



$$\text{eq.2} \Rightarrow 20 = 16 I_2 + 3 I_1 \Rightarrow I_2 = \frac{20 - 3 I_1}{16}$$

$$\text{eq.3} \Rightarrow 20 = 6 I_3 + 3 I_1 \Rightarrow I_3 = \frac{20 - 3 I_1}{6}$$

$$I_1 = I_2 + I_3$$

$$\Rightarrow I_1 = \frac{20 - 3 I_1}{16} + \frac{20 - 3 I_1}{6}$$

$$\Rightarrow I_1 = \frac{6 \times (20 - 3 I_1) + 16 \times (20 - 3 I_1)}{16 \times 6}$$

$$\Rightarrow I_1 = \frac{6 \times 20 - 6 \times 3 I_1 + 16 \times 20 - 16 \times 3 I_1}{16 \times 6}$$

$$\Rightarrow I_1 = \frac{440 - 66 I_1}{96} \Rightarrow 96 I_1 + 66 I_1 = 440 \Rightarrow 162 I_1 = 440 \Rightarrow I_1 = \frac{440}{162} \Rightarrow I_1 = 2.72 \text{ A}$$


$$I_2 = \frac{20 - 3 I_1}{16}$$

$$\Rightarrow I_2 = \frac{20 - 3 \times 2.72}{16} \Rightarrow I_2 = 0.74 \text{ A}$$

$$I_1 = I_2 + I_3 \Rightarrow I_3 = I_1 - I_2 = 2.72 - 0.74 \Rightarrow I_3 = 1.98 \text{ A}$$

EXERCISE 06

The current through each branch.

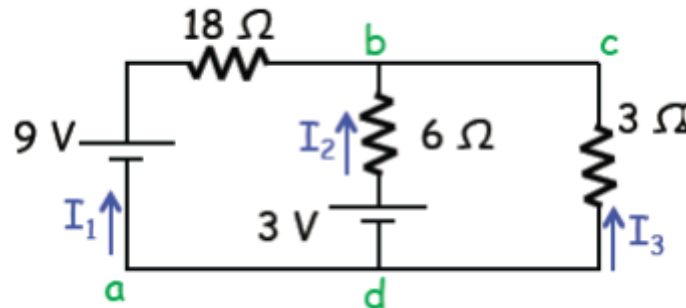

According to Kirchhoff's Current Law:

$$I_1 + I_2 + I_3 = 0 \dots \dots \dots \text{eq.1}$$

According to Kirchhoff's Voltage Law:

From loop 1:

$$9 \text{ V} = 18 I_1 - 6 I_2 + 3 \text{ V} \dots \dots \dots \text{eq.2}$$

From loop 2:

$$3 \text{ V} = 6 I_2 - 3 I_3 \dots \dots \dots \text{eq.3}$$

$$\text{eq.2} \Rightarrow 6 = 18 I_1 - 6 I_2 \Rightarrow I_1 = \frac{6 + 6 I_2}{18} \Rightarrow I_1 = \frac{1 + I_2}{3}$$

$$\text{eq.3} \Rightarrow 3 = 6 I_2 - 3 I_3 \Rightarrow I_3 = \frac{-3 + 6 I_2}{3}$$

$$\begin{aligned} I_1 + I_2 + I_3 &= 0 \\ \Rightarrow \frac{1 + I_2}{3} + I_2 + \frac{-3 + 6 I_2}{3} &= 0 \\ \Rightarrow \frac{1 + I_2 + 3 I_2 - 3 + 6 I_2}{3} = 0 \Rightarrow I_2 &= \frac{2}{10} \Rightarrow I_2 = 0.2 \text{ A} = 200 \text{ mA} \end{aligned}$$

$$I_1 = \frac{1 + I_2}{3} \Rightarrow I_1 = \frac{1 + 0.2}{3} \Rightarrow I_1 = 0.4 \text{ A} = 400 \text{ mA}$$

$$I_3 = \frac{-3 + 6 I_2}{3} \Rightarrow I_3 = \frac{-3 + 6 \times 0.2}{3} \Rightarrow I_3 = -0.6 \text{ A} = -600 \text{ mA}$$

I_3 : is in the opposite direction: $I_1 + I_2 = I_3$