

University of M 'sila

Faculty of: Technology

Common Base

Forth Series Of Exercises - Phys 02

Exercise 01: Fig.01

A conducting sphere of radius $R_1 = R$ centered in O , carry a charge $- 2Q$ surrounded by a conducting shell with inner radius $R_1 = 1.5R$ and outer radius $R_1 = 2R$ carrying a charge $- Q$

1/ What is the charge distribution of the shell when it is in electrostatic equilibrium

2/ Using Gauss' Law, find the electric field $\vec{E}(\mathbf{r})$ at everywhere in space.

3/ Deduce the potential $V(\mathbf{r})$ at everywhere in space.

4/ Plot $E(\mathbf{r})$ and $V(\mathbf{r})$

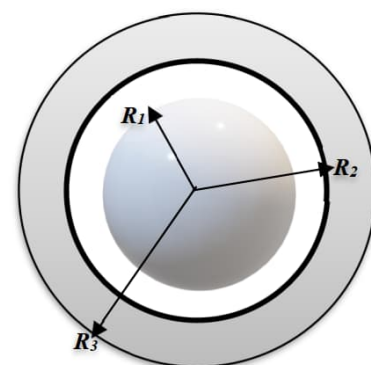


Fig .01

Exercise 02: Fig.02

4 capacitors $C_1 = 15 \mu F$, $C_2 = 3 \mu F$, $C_3 = 6 \mu F$ and $C_4 = 20 \mu F$ are connected to the voltage source of e.m.f $\epsilon = 15 V$ in the configuration of fig 02.

1/ What is the equivalent capacitance?

2/ Calculate the charge Q_i and the potential difference V_i for each capacitor.

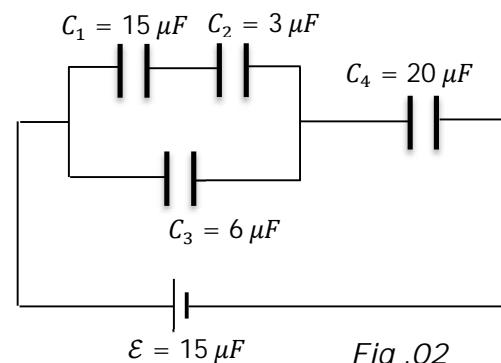


Fig .02

Exercise 03: Fig.03

Let the circuit of the figure 03. Using the Kirchhoff's Law,

1/ Calculate the current in different branches.

2/ What is the potential difference for each resistor?

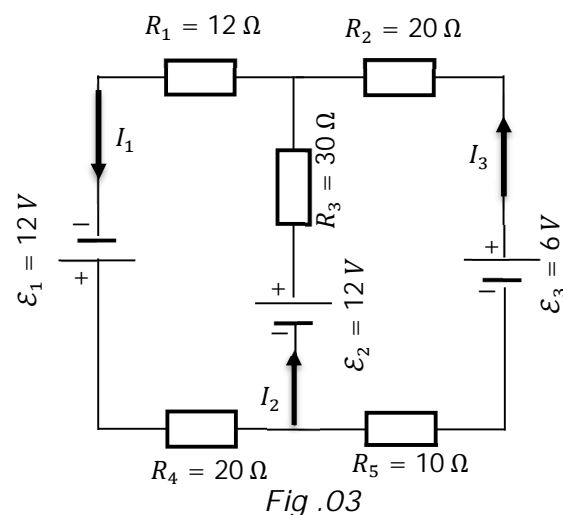


Fig .03

Exercise 04: Fig.04

Let the circuit of the figure 04. Using the Kirchhoff's Law,

- 1/ Calculate the current in different branches.
- 2/ Find is the potential difference for each resistor?

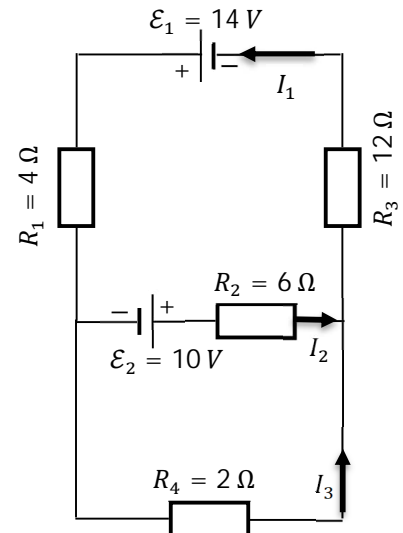



Fig .04

Exercise 05: Additional Fig.05

In the circuit of the figure 05, for capacitors $C_1 = C_3 = 1 \mu F$ and $C_2 = C_4 = 2 \mu F$ are connect to the voltage source of e.m.f $\mathcal{E} = 24 V$

1/ Find the equivalent capacitance, the charge and the protentional difference for each condenser in the following cases:

- Switch S open
- Swich S close

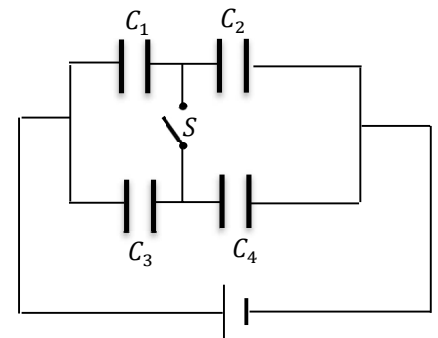

$\mathcal{E} = 24 \mu F$

Fig .05

Exercise: 06

Five resistors $R_1 = 1 k\Omega$, $R_2 = R_4 = 2 k\Omega$, $R_3 = 4 k\Omega$, and a variable resistance r , are connected as seen in figure 06

- 1/ Express the equivalent resistance as function of r (between A and B)
- 2/ What is the value of r for which the value of equivalent resistance is equal to r ?

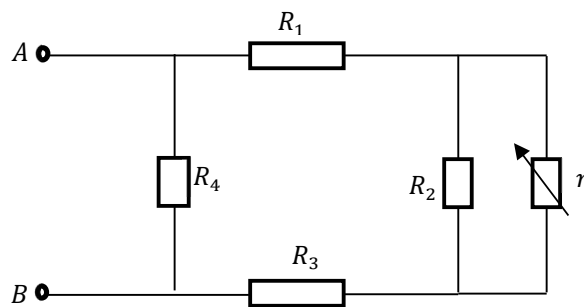


Fig .06