

TD 1 : Continuous regime and fundamental theorems

Exercise N°1 : Current divider

From the circuit in Figure 1 opposite, determine

- 1/ The equivalent resistance seen from points a and b.
- 2/ The current supplied by source V_f .
- 3/ the current flowing through each of the resistors R_1 and R_2 .

Data : $V_f = 18V$, $R_1 = 7\Omega$, $R_2 = 2\Omega$

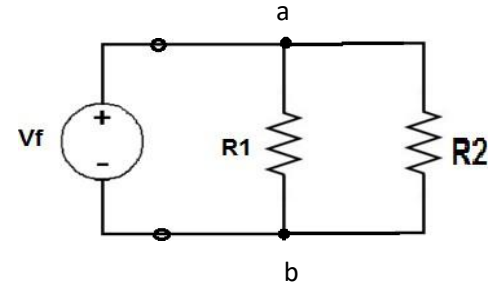


Figure 1

Exercise N°2 : Voltage divider

Determine for the circuit in Figure 2 below, by applying the voltage divider, the current i flowing through resistor R_2 and the voltage u across resistor R_3 :

Data : $E = 6V$, $R_1 = 100\Omega$, $R_2 = R_3 = R_4 = 50\Omega$

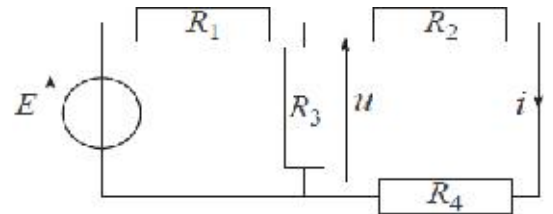


Figure 2

Exercise N°3 : Linear circuit

- 1) In the circuit in Figure 3 opposite:
- 2) 1) Calculate U_{EF},
- 3) 2) Calculate the intensity I_0 flowing in the main branch.
- 4) 3) Calculate the intensity I' flowing in the branch containing the generator E' (specify its direction);
- 5) 4) Calculate the intensities i_1 , i_2 and i_3 .

Data : $R = 1\Omega$, $E = 5V$ et $E' = 3V$.

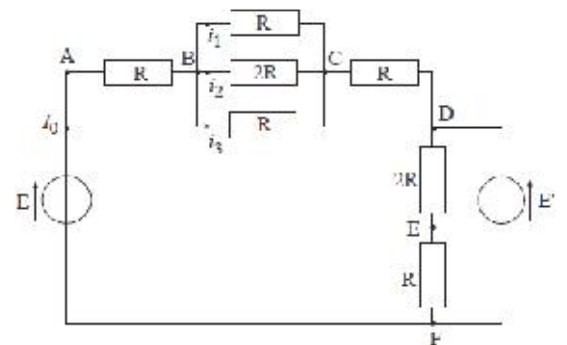


Figure 3

Exercise N°4 : KIRCHHOOF Voltage Law (KVL)

Determine the currents of the meshes i_1 and i_2 in the circuit of the Figure 4


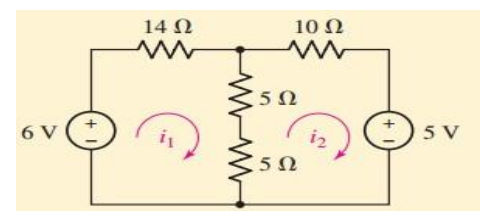


Figure 4

Exercise N°5 : Kramer's method

Use mesh analysis to determine the mesh currents of the circuit **Figure 5**

Figure 5

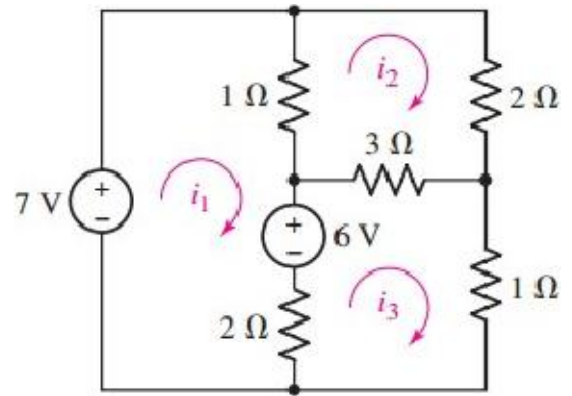

Exercise N°6 : Kirchhoff/ Superposition / Millman

Calculate the current intensity in branch AB of Figure 6 by applying:

- 1) Kirchhoff's laws.
- 2) The superposition theorem.
- 3) Millman's theorem


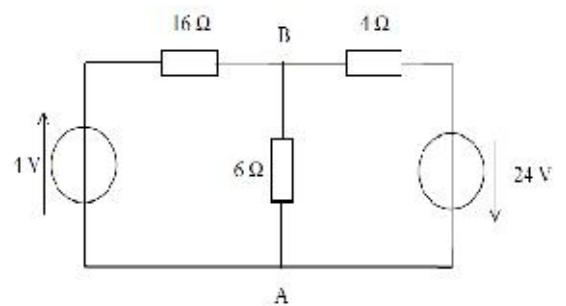


Figure 7

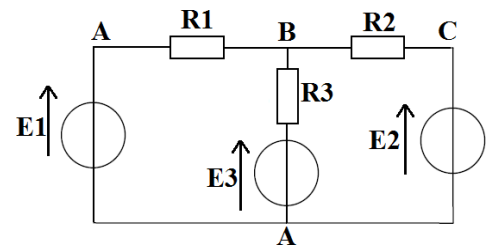Exercise N°7: Superposition


The circuit includes two generators ($E_1 = 20\text{ V}$, $R_1 = 3\ \Omega$, $E_2 = 15\text{ V}$, $R_2 = 4\ \Omega$) supplying a motor ($E_3 = 8\text{ V}$, $R_3 = 5\ \Omega$) Figure 7.

Determine the value of the current intensity in R_3 by applying the superposition theorem.



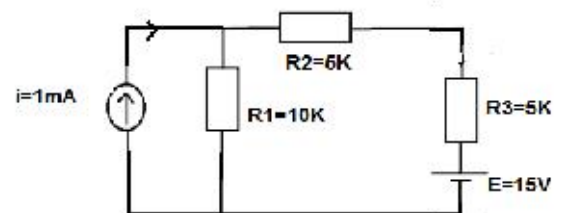Exercise N°8 : Superposition

Using the superposition theorem, determine the voltage across resistor R_1 in Figure 8.



Exercice N°9 : Voltage source – current source transformation

Consider the assembly in Figure 9 below.
Calculate the electric current I flowing through the operating resistance R_U .

Data : $I_1 = 2 \text{ mA}$, $I_2 = 5 \text{ mA}$
, $R_1 = 10 \text{ k}\Omega$ et
 $R_2 = 5 \text{ k}\Omega$.

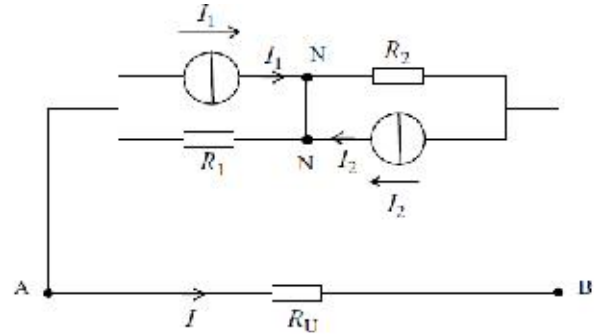


Figure 9

Exercice N°10 : Voltage source – current source transformation

- 1- Reduce the circuit of Figure 10 to an equivalent dipole comprising a voltage source V_{eq} in series with a resistor R_{eq} (dipole “equivalent voltage source”).
2. If we connect to port 11’ a load resistor $R_L = 10 \Omega$, calculate the power absorbed by R_L .

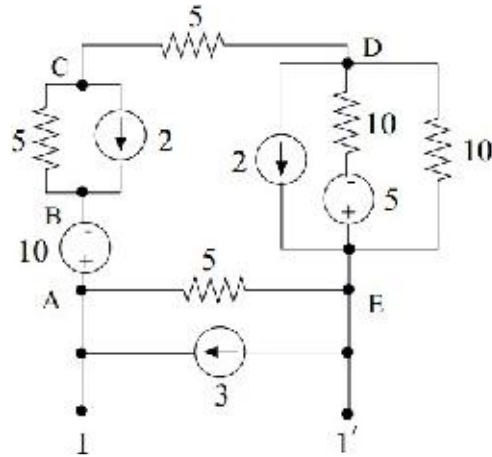


Figure 10

Exercice N°11 : THEVENIN

Determine the Thevenin generator of the following Figure 11, without taking into account the resistance R .


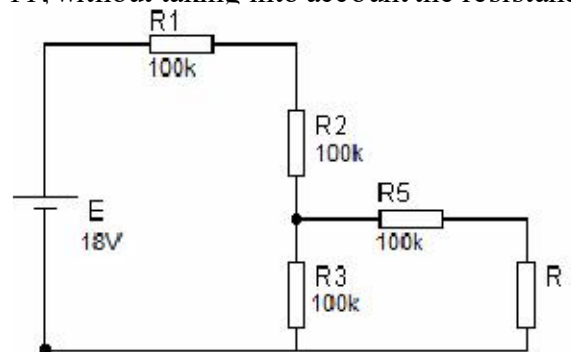


Figure 11

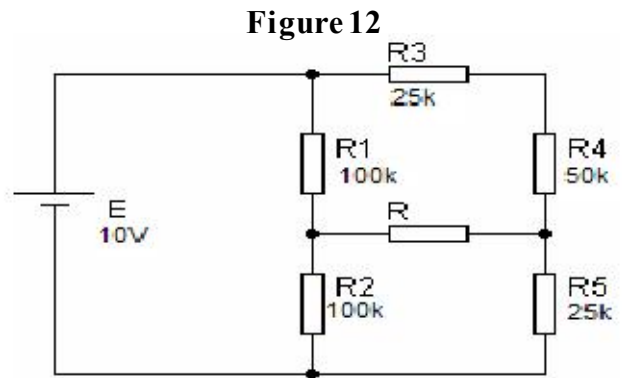Exercise N°12 : THEVENIN

In the assembly of Figure 12 below, determine the current I flowing in the resistor $R = 100k$.



Exercise N°13 : THEVENIN

Give the Thevenin generator of Figure 13 below, without taking into account the resistance R .

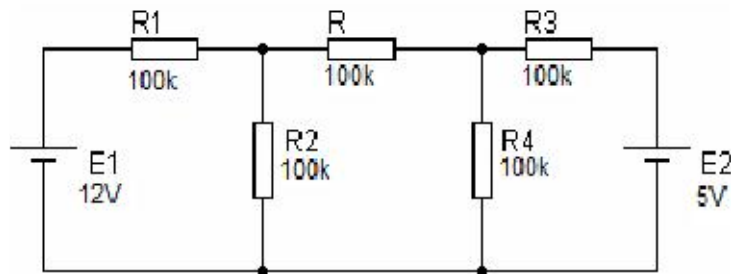


Figure 13


Exercise N°14 : NORTON

Consider the electrical circuit given by Figure 14 below:

We give: $E = 8\text{ V}$; $R_1 = 4\ \Omega$; $R_2 = 12\ \Omega$; $R_3 = 9\ \Omega$


Calculate the current I which crosses the resistor R_3 by applying Norton's theorem.

Figure 14

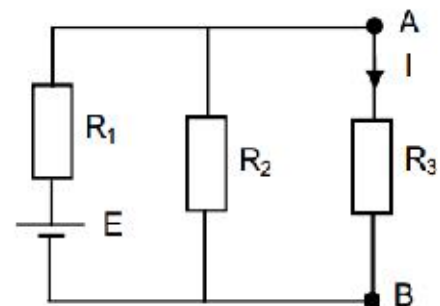

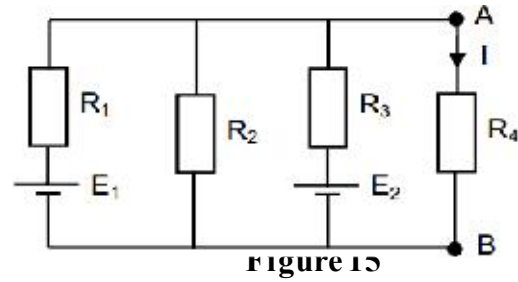
Exercise N°15 : NORTON

Consider the electrical circuit given by Figure 15 below: We give: $E_1 = 10V$; $E_2 = 5V$; $R_1 = R_3 = R_4 = 100 \Omega$; $R_2 = 50 \Omega$. Calculate the current I by applying Norton's theorem,



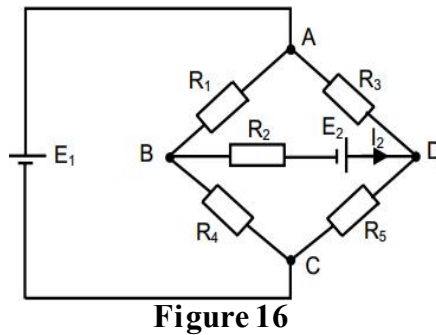Exercise N°16 NORTON

Consider the electrical circuit given by Figure 16 below: We give: $E_1 = 10V$; $E_2 = 2V$; $R_1 = 60 \Omega$; $R_3 = 120 \Omega$; $R_4 = 180 \Omega$; $R_2 = 240 \Omega$; $R_5 = 90 \Omega$. Calculate the current I by applying Norton's theorem,



Exercise N°17 KENNELY

Determine the equivalent resistance R_T of the dipole AD of the following network using the network conversion rules. $R_1 = 2\Omega$, $R_2 = 4\Omega$, $R_3 = 6\Omega$, $R_4 = 5\Omega$, $R_5 = 4\Omega$. Figure 17.

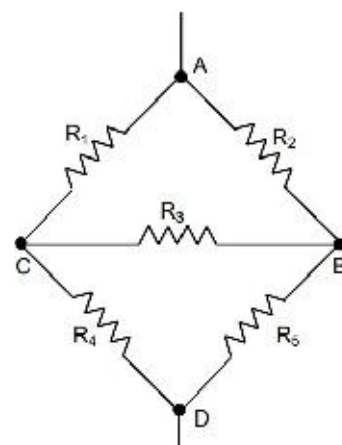


Figure 17

Exercise N°18 Controlled source

Calculate the value of the voltage source V_s in Figure 18 if the current I_ϕ is equal to 5 A.

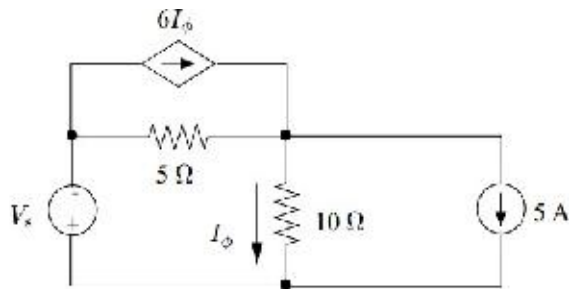


Figure 18

Exercise N°19 Controlled source

Determine the current i_1 in the circuit of the **Figure 19**

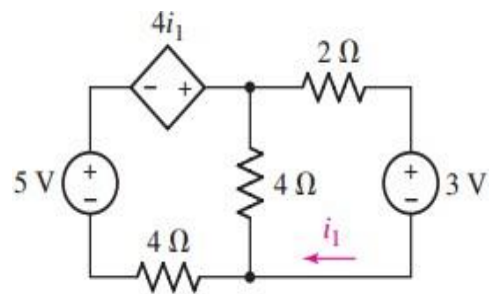


Figure 19

Exercise N°20 Controlled source

Applying the superposition theorem, determine the current i_x in Figure 20

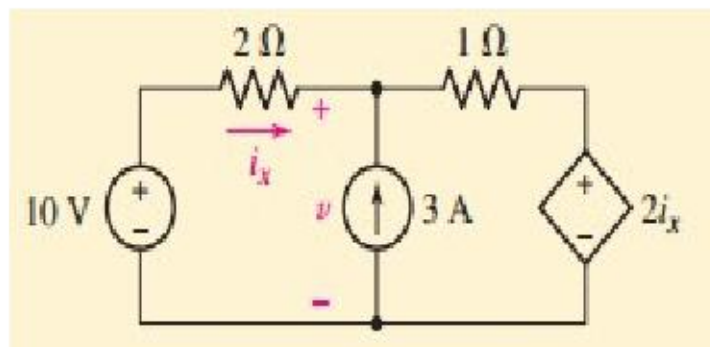


Figure 20