

**People's Democratic Republic of Algeria**  
**Ministry of Higher Education and Scientific Research**  
**Mohamed Boudiaf University of M'sila**  
**Faculty of Sciences**

**Common Trunk of Matter Sciences**

**Practical works - Physics 2**

**1<sup>st</sup> year - 2<sup>nd</sup> semester**

## **4<sup>th</sup> Practical Work**

# **Resistance Measurement**

**Experiment date:** ...../...../.....

**Corrector professor :** .....

**Report prepared by :**

<b>First name</b>	<b>Family name</b>	<b>Group</b>	<b>Sup-group</b>	<b>Preparation mark</b>	<b>Final mark</b>
				<b>/5,00</b>	<b>/20,00</b>
				<b>/5,00</b>	<b>/20,00</b>
				<b>/5,00</b>	<b>/20,00</b>
				<b>/5,00</b>	<b>/20,00</b>
				<b>/5,00</b>	<b>/20,00</b>
				<b>/5,00</b>	<b>/20,00</b>
				<b>/5,00</b>	<b>/20,00</b>

***Academic year : 2023/2024***

## 1-The purpose of experiment

The purpose of this experiment is to measure current, voltage and resistance using a multimeter. Calculate Resistance using Ohm's law. Assemble the setup of simple and mixed electrical circuits. Determine the equivalent resistance of a mixed circuit. Check the law of junctions and the law of loops. Highlight the usefulness and use of the Wheatstone bridge and Knowledge of metals from the measurement of resistivity.

## 2-Notions and preparation work

### 2-1- Some laws of electrical circuits

Let a circuit consist of a generator ( $E$ ) connected to a resistor  $R$  (expressed in Ohms) using the conductive wires (figure-1).

Voltage is responsible for the movement of charges in an electrical circuit, the current is the flow of these charges, and resistance represents the tendency of a circuit element

to oppose the flow of current.

The voltage  $V$  (expressed in Volts) is measured using a voltmeter « $V$ ». It is a parallel measurement with an element of the circuit.


The current  $I$  (expressed in Amps) is measured using an ammeter « $A$ ». It is a series measurement in the circuit. According to Ohm's law, measurements made against a resistor must satisfy the relationship:  $V = RI$ ,

A group of resistances ( $R_1, R_2, \dots, R_n$ ) in series has an equivalent resistance given by  $R_{eq} = R_1 + R_2 + \dots + R_n$ , while  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$  when these resistors are connected in parallel.


- Calculate the equivalent resistance for  $R_1 = 100\Omega$ ,  $R_2 = 150\Omega$ , and  $R_3 = 100\Omega$ .

2-1-a- $R_1, R_2$  and  $R_3$  are connected in series,  $R_{eq} = \dots \Omega$ .

2-1-b- $R_1, R_2$  and  $R_3$  are connected in parallel,  $R_{eq} = \dots \Omega$

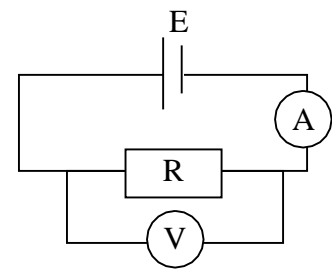

**Figure-1**

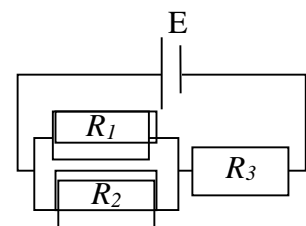

**figure-2**

2-1-c- $R_1, R_2$  and  $R_3$  are connected in a mixed circuit


according to figure-2;  $R_{eq} = \dots \Omega$ .

**Note:** The equivalent resistance is calculated from the equivalent circuit where each branch is replaced by a resistance by first simplifying the series resistance groupings.

2-1-d- $R_1, R_2$  and  $R_3$  are mounted in a mixed circuit according to Figure-3;  $R_{eq} = \dots \Omega$ .

-The law of junctions applies to connection points of circuit elements. The law of junctions states that the sum of the currents entering a junction is equal to the sum of the currents leaving the junction.

For the mixed circuit following figure-3;  $I = I_1 + I_2$ .

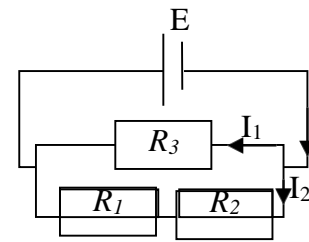

**Figure-3**

The law of meshes applies to loops in the electrical circuit. The law of meshes states that the sum of currents entering a node is equal to the sum of the currents leaving the node. (figure-4). For the previous circuit, we have


Mesh  $N^01$  traveled by the current  $I_1$ :

$$E = R_3 I_1 = R_3 (I - I_2)$$

Mesh  $N^02$  traveled by the current  $I_2$ :

$$0 = -R_3 I_1 + (R_1 + R_2) I_2 = R_3 (I_2 - I) + (R_1 + R_2) I_2$$

where  $E$  is the voltage across the generator.

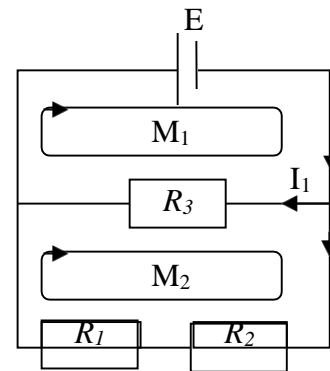

**Figure-4**

### 2-2- Wheatstone bridge

The Wheatstone bridge is used to convert a variation in resistance into a variation in voltage, which makes it a sensor in environments where measurement is difficult.

Consider the setup of figure-5.

2-2-a- Give the direction of  $U_{AM}, U_{BM}, U_{AB}$  in figure-5.

2-2-b- Express  $U_{AM} = f(R_1, R_2, E)$

$$U_{AM} = \dots$$


2-2-c- Express  $U_{BM} = f(R_v, R_x, E)$

$$U_{BM} = \dots$$

2-2-d- Deduce  $U_{AB} = f(R_1, R_2, R_v, R_x, E)$

$$U_{AB} = \dots$$

2-2-c-If  $U_{AB} = 0$ , the bridge is said to be equilibrated.

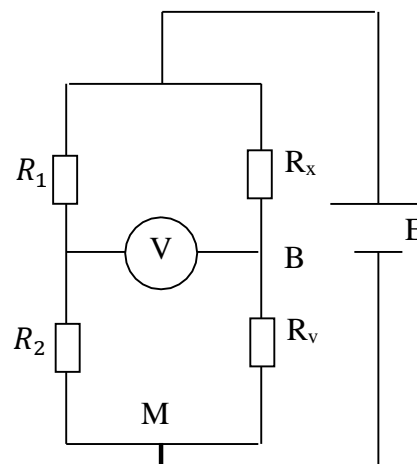

**Figure-5**

Show that the expression for  $R_x$  takes a form independent of the supply voltage.

.....

**3- Practical work**

**3-1- Simple circuits**

**3-1-a- Resistors in series**

Perform the setup where  $R_1, R_2$  and  $R_3$  are

Connecting in series.

Powering your circuit with voltage  $E = 5.0V$  and complete the opposite table.

	$R_1$	$R_2$	$R_3$
$I (mA)$			
$V(Volts)$			
$Resistance (\Omega)$			

**3-1-b- Resistors in parallel**

Perform the setup where  $R_1, R_2$  and  $R_3$  are

Connecting in parallel.

Powering your circuit with voltage  $E = 5.0V$  and complete the opposite table

	$R_1$	$R_2$	$R_3$
$I (mA)$			
$V(Volts)$			
$Resistance (\Omega)$			

**3-2-Mixed circuits**

Perform the setup where  $R_1, R_2$  and  $R_3$  are following figure-2.

Powering your circuit with voltage  $E = 5.0V$  and complete the opposite table

	$R_1$	$R_2$	$R_3$
$I (mA)$			
$V(Volts)$			
$Resistance (\Omega)$			

Perform the setup where  $R_1, R_2$  and  $R_3$  are following figure-3.

Powering your circuit with voltage  $E = 5.0V$  and complete the opposite table

	$R_1$	$R_2$	$R_3$
$I (mA)$			
$V(Volts)$			
$Resistance (\Omega)$			

**3-3- Measuring the resistivity of a material**

Perform the experimental setup in figure -5, where  $R_1 = 1 k\Omega$  and  $R_2 = 100k\Omega$  and the resistant wire in place of  $R_x$ . Power the circuit with a voltage  $E=5.0V$ .

Vary the resistance " $R_v$ " until the bridge is equilibrated (the galvanometer indicates zero voltage). For different section values,  $S$ , of resistant wire " $L = 1 m$ " long;

a)-Complete the table opposite.

Wire diameter $d (mm)$	1	0.5	0.7
$R_v (\Omega)$			
Resistance $R_x (\Omega)$			
Resistivity $\rho = \frac{RS}{L}$ ( $\Omega.cm$ )			

b)-Deduce the type of the two metals; Use the displayed table of resistivity values.

.....

**Electrical resistivity values of certain materials (at T=20°C)**

<b>Material</b>	<b>Resistivity (x 10<sup>-6</sup> Ω .cm)</b>
<b>Silver</b>	<b>1.63</b>
<b>Copper</b>	<b>1.69</b>
<b>Gold</b>	<b>2.2</b>
<b>Aluminum</b>	<b>2.67</b>
<b>Tungsten</b>	<b>5.4</b>
<b>Zinc</b>	<b>5.96</b>
<b>Brass (copper + zinc alloy)</b>	<b>6.2-7.8</b>
<b>Iron</b>	<b>10.1</b>
<b>Platinum</b>	<b>10.58</b>
<b>Lead</b>	<b>20.6</b>
<b>Constantan (Cu55/Ni45 alloy)</b>	<b>52</b>
<b>Carbon</b>	<b>3500</b>
<b>Germanium</b>	<b>46 x10<sup>6</sup></b>
<b>Silicon</b>	<b>23 x10<sup>6</sup></b>
<b>Glass</b>	<b>10<sup>10</sup> - 10<sup>14</sup></b>
<b>Hard rubber</b>	<b>10<sup>13</sup></b>
<b>Suffer</b>	<b>10<sup>15</sup></b>
<b>Fused Quartz</b>	<b>76 x10<sup>16</sup></b>