

**People's Democratic Republic of Algeria**  
**Ministry of Higher Education and Scientific Research**  
**Mohamed Boudiaf University of M'sila**  
**Faculty of Sciences**

**Common Trunk of Matter Sciences**  
**1<sup>st</sup> year - 2<sup>nd</sup> semester**

**Practical works - Physics 2**

**3<sup>rd</sup> Practical Work**

**Charging and Discharging of  
Capacitor**

**Experiment date:** ...../...../.....

**Corrector professor :** .....

**Report prepared by :**

<b>First name</b>	<b>Family name</b>	<b>Group</b>	<b>Sup- group</b>	<b>Preparation mark</b>	<b>Final mark</b>
				<b>/5,00</b>	<b>/20,00</b>
				<b>/5,00</b>	<b>/20,00</b>
				<b>/5,00</b>	<b>/20,00</b>
				<b>/5,00</b>	<b>/20,00</b>
				<b>/5,00</b>	<b>/20,00</b>
				<b>/5,00</b>	<b>/20,00</b>
				<b>/5,00</b>	<b>/20,00</b>

**Academic year : 2023/2024**



$$U_C = E.e^{-\frac{t}{RC}} \Rightarrow i(t) = -\frac{E}{R}e^{-\frac{t}{RC}}$$

.....

.....

.....

.....

.....

.....



.....

.....

.....

.....

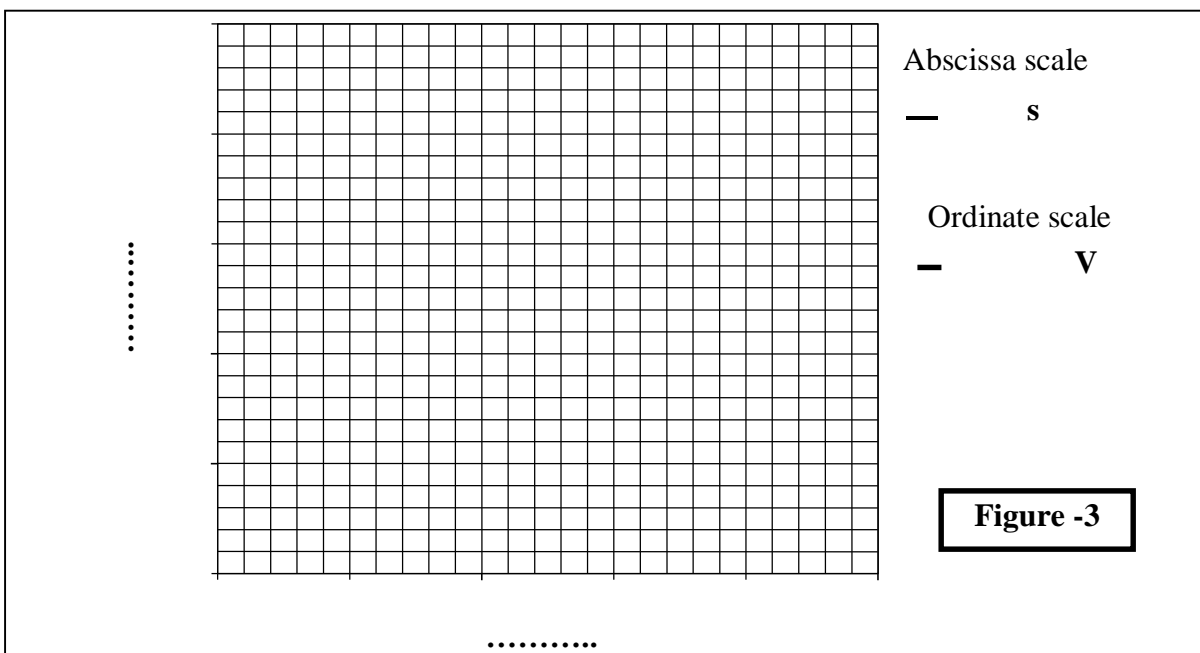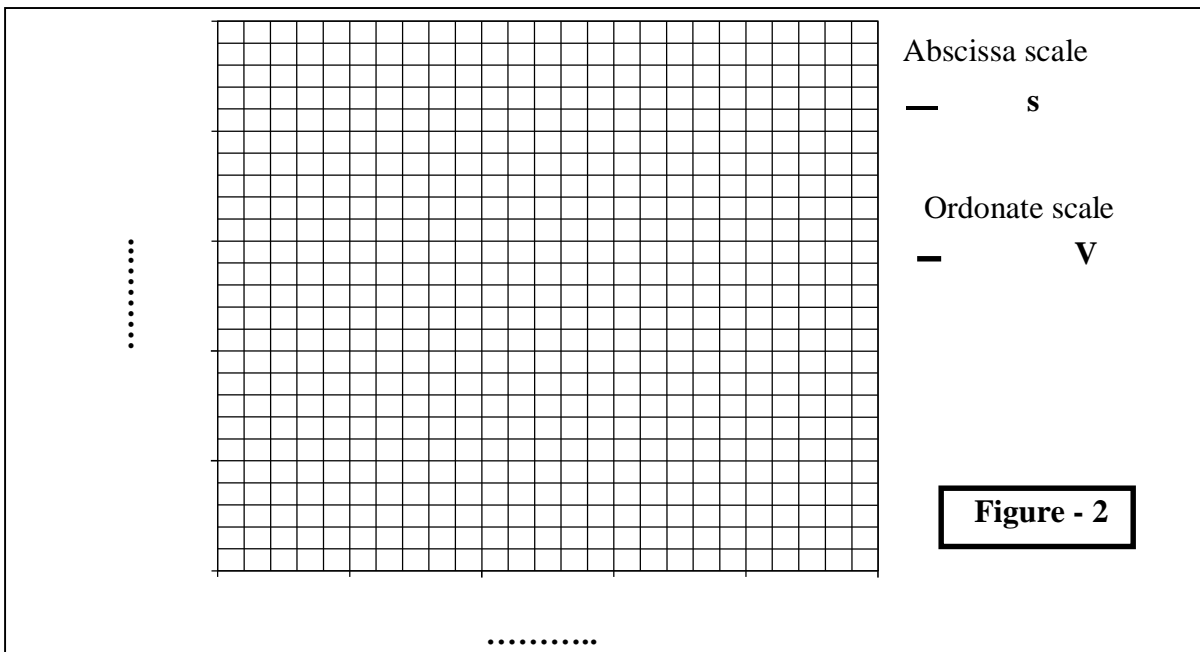c- Draw the curve of  $U_C = f(t)$  (figure-3).



**3-Practical work**

**3-1- Charge of a capacitor**

Before connecting the capacitor, make sure it is discharged by short-circuiting it. Perform the setup in figure-1 with the switch in position 1 for resistance «  $R=3.3M\Omega$  » and a capacitor with capacity «  $C=2 \mu F$  ».

Start counting time with a stopwatch simultaneously with powering the circuit with a DC voltage source  $E=8 V$ .

Read the voltage of the terminals capacitor each « 05 seconds ».


Record the values in the following table :

$t (s)$	00	05	10	15	20	25	30	35	40	45	50
$U_C (Volt)$											

a- Plot the voltage  $U_C = f(t)$  (figure-4).

b- Plot the tangent to the origin and determine the time constant  $\tau = RC$  ; the abscissa of the point of intersection of this tangent with the load limit voltage.  $\tau = \dots\dots\dots$

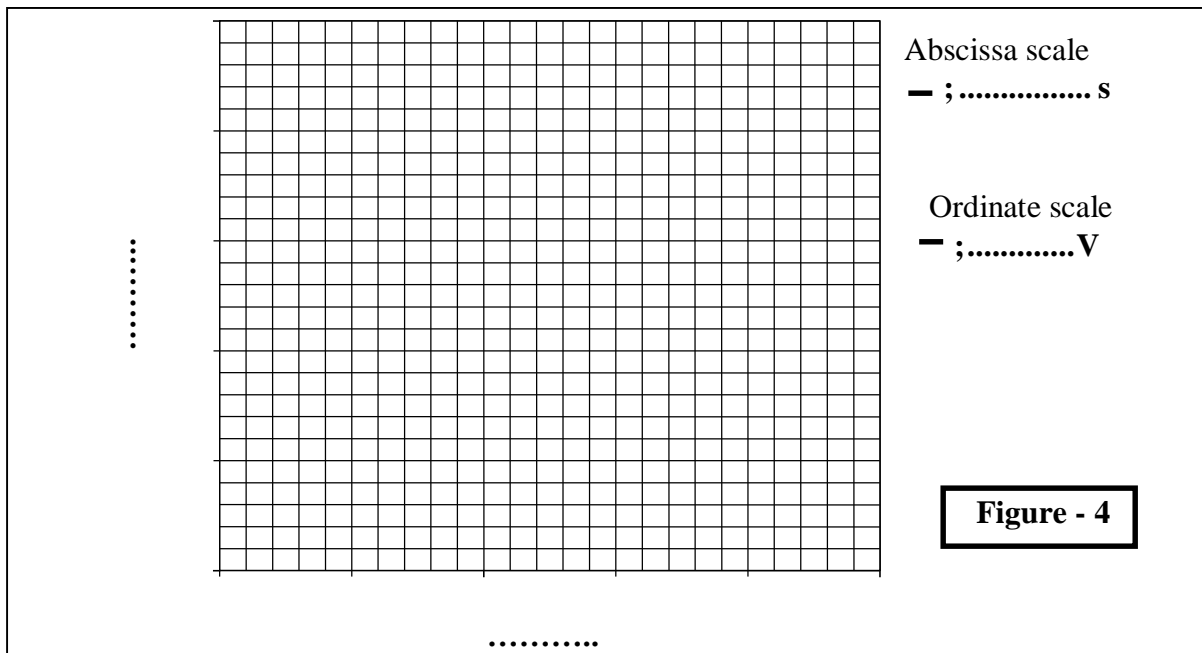c- From the time constant ensure the value of  $C$ .  $C = \dots\dots\dots \mu F$



**3-2- Discharge of a capacitor**

In the case of charging the capacitor being charged, we will disconnect the voltage source while letting the discharge take place through the resistance R «Switch in position 2 ».

Start counting time with a stopwatch simultaneously when disconnecting power from the circuit.

Read the voltage of the terminals capacitor each « 05 seconds ».


Record the values in the following table:

$t$ (s)	00	05	10	15	20	25	30	35	40	45	50
$U_C$ (Volt)											

a- Plot the tension  $U_c = f(t)$  (figure-5).

b- Plot the tangent to the discharge point and determine the time constant  $\tau = RC$ ; the abscissa of the point of intersection of this tangent with the load limit voltage.  $\tau = \dots\dots\dots$

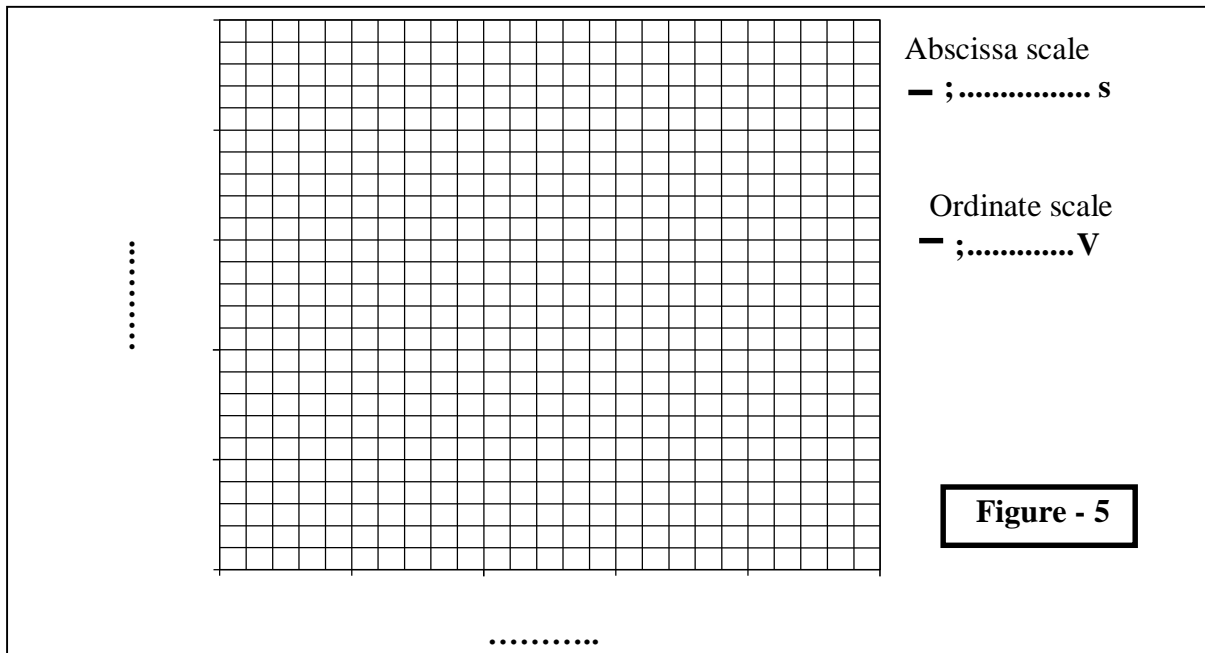c- From the time constant ensure the value of  $C$ .  $C = \dots\dots\dots \mu F$




**3-3- Association of capacitors in parallel**

Perform the experimental setup in figure-6 for resistance «  $R = 3.3 M\Omega$  » and two capacitor of capacities «  $C_1 = 1 \mu F$ ;  $C_2 = 1 \mu F$  ».

Start counting time with a stopwatch simultaneously with powering the circuit with a DC voltage source  $E = 8 V$ .

Read the voltage of the terminals capacitor each 05 seconds.

Record the values in the following table :

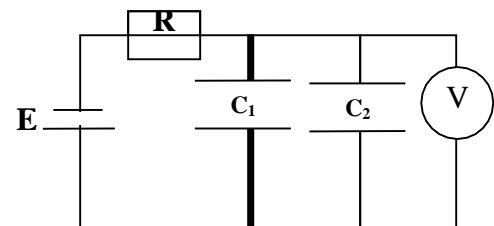

**Figure-6**

$t$ (s)	00	05	10	15	20	25	30	35	40	45	50
$U_C$ (Volt)											

a-Plot the voltage  $U_c = f(t)$  (figure-7).


b-Plot the tangent to the discharge point and determine the time constant  $\tau = R.C$  the abscissa of the point of intersection of this tangent with the load limit voltage.  $\tau = \dots\dots\dots$

c- From the time constant determine the value of  $C$ .  $C = \dots\dots\dots \mu F$ .

d- Compare this value to the equivalent value for two capacitors in parallel


$$C_{eq} = C_1 + C_2$$

.....

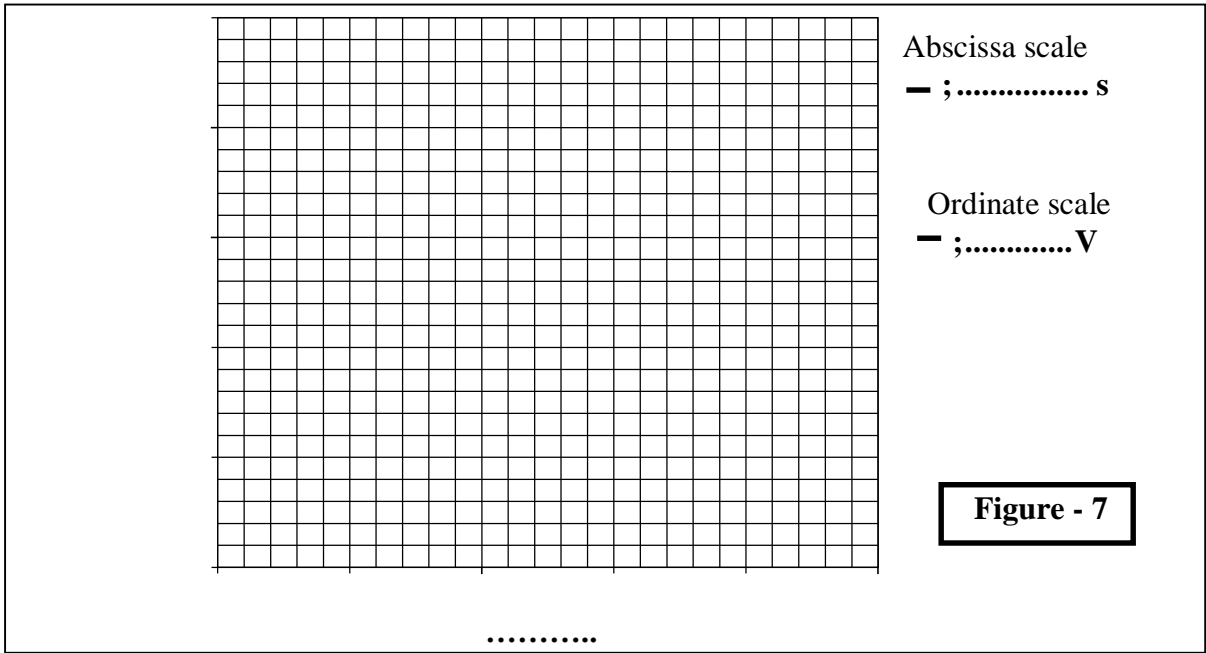

**3-4- Association of capacitors in series**

Perform the setup in figure-8 for resistance «  $R=3.3M\Omega$  » and two capacitors of capacities «  $C_1=6 \mu F$  ;  $C_2=3 \mu F$  » and this after having discharged by short circuit. Start counting time with a stopwatch simultaneously with powering the circuit with a DC voltage source  $E=8 V$ .

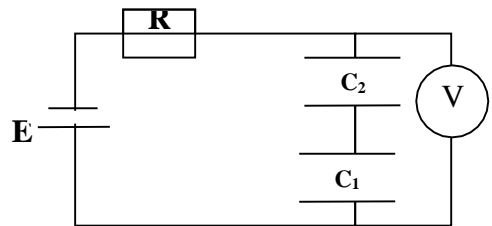

**Figure-8**

Read the voltage of the the terminals capacitor each « 05 seconde »

Record the values in the following table :

$t$ (s)	00	05	10	15	20	25	30	35	40	45	50
$U_c$ (Volt)											

a- Plot the voltage  $U_c = f(t)$  (figure-9).

b- Plot the tangent to the discharge point and determine the time constant  $\tau = R.C$  the abscissa of the point of intersection of this tangent with the load limit voltage.  $\tau = \dots$

c- From the time constant determine the value of  $C$ .  $C = \dots \mu F$ .

Compare this value to the equivalent value for two capacitors in series:

$$C_{eq} = C_1 C_2 / (C_1 + C_2)$$

.....

