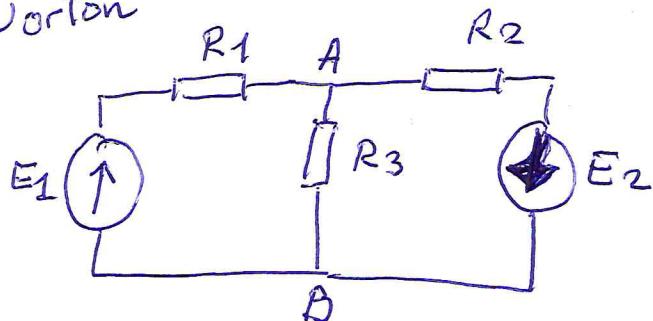


EX: Calculer la tension  $V_{AB}$  du circuit suivant  
En utilisant les Théorèmes de  
Millman - superposition - Thévenin

Norton






page 1

Millman

$$V_{AB} = \frac{\frac{E_1}{R_1} - \frac{E_2}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

2. Superposition

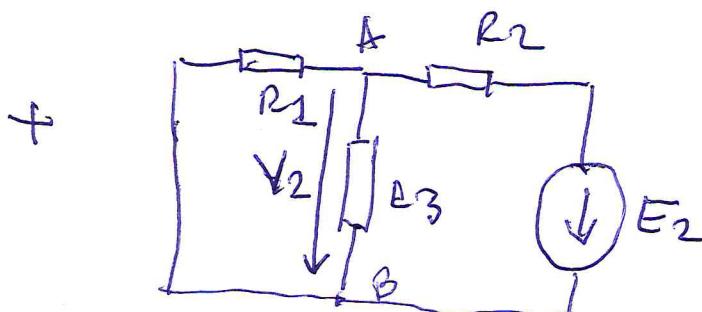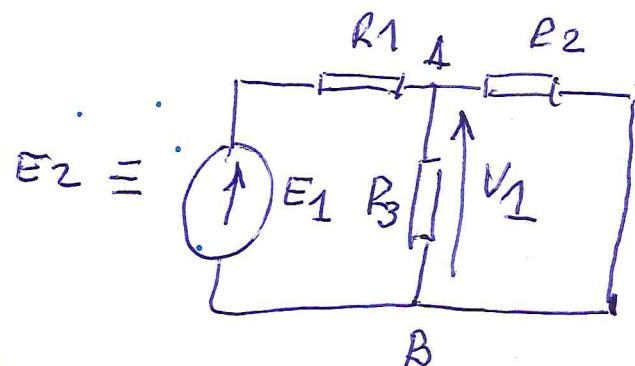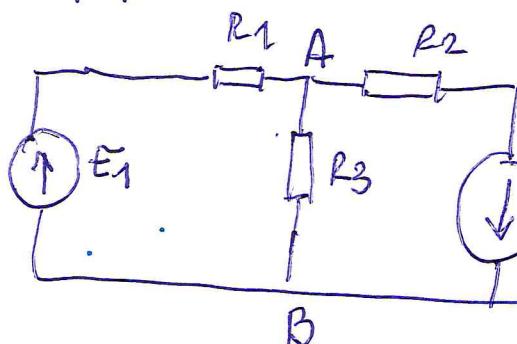

$$V_1 = \frac{\frac{R_2 R_3}{R_2 + R_3}}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} E_1$$

$$= \frac{\frac{R_2 R_3}{R_2 + R_3}}{R_1 R_2 + R_1 R_3 + R_2 R_3} E_1 = \frac{R_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3} E_1$$


$$V_2 = \frac{\frac{R_1 R_3}{R_1 + R_3}}{R_2 + \frac{R_1 R_3}{R_1 + R_3}} \cdot E_2$$

$$V_2 = \frac{\frac{R_1 R_3}{R_1 + R_3} \cdot E_2}{\frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1 + R_3}} = \frac{R_1 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3} \cdot E_2$$



$$V_{AB} = V_1 - V_2 = \frac{R_2 R_3 E_1}{R_1 R_2 + R_2 R_3 + R_1 R_3} - \frac{R_1 R_3 E_2}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

$$V_{AB} = \frac{R_2 R_3 E_1 - R_1 R_3 E_2}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

Théorème de Thévenin :

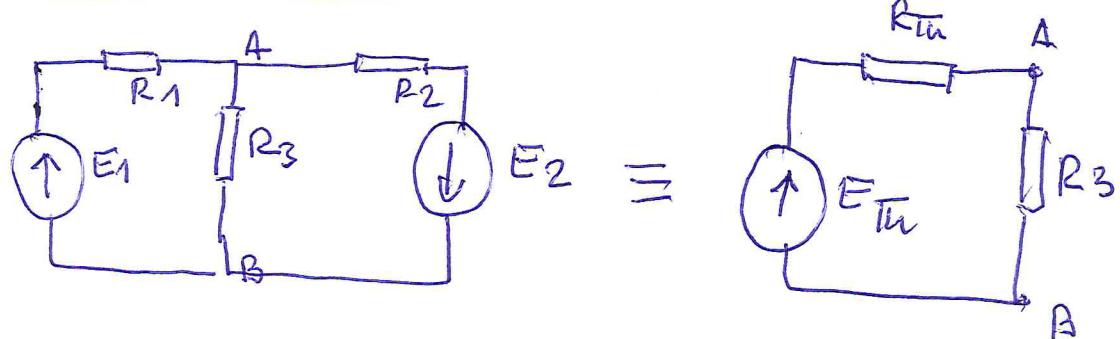


$$E_{Th} = V_{AB}$$

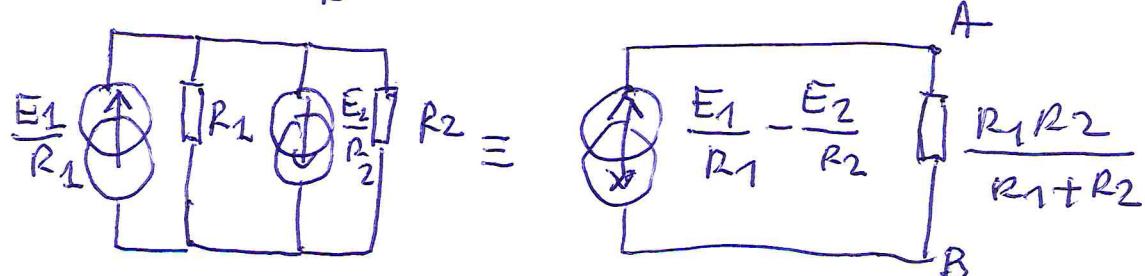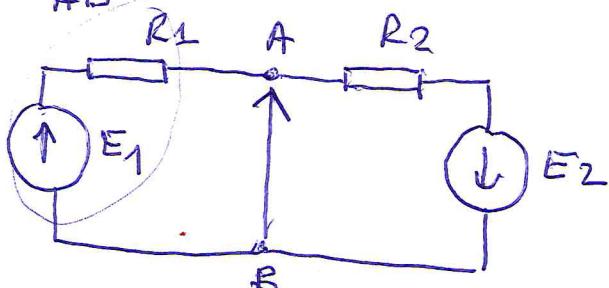

$$V_{AB} = \left( \frac{E_1}{R_1} - \frac{E_2}{R_2} \right) \frac{R_1 R_2}{R_1 + R_2}$$

$R_{Th} = ?$

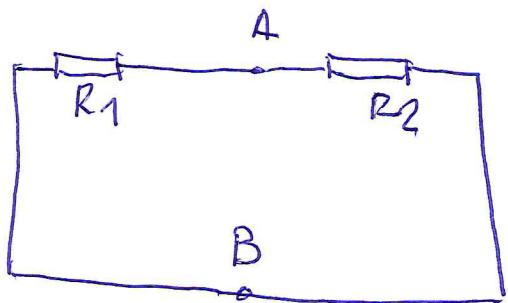

$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2}$$

oder

$$V_{AB} = \frac{R_3}{R_3 + R_m} \cdot E_{Th}$$

$$= \frac{R_3}{R_3 + \frac{R_1 R_2}{R_1 + R_2}} \cdot \left( \frac{E_1}{R_1} - \frac{E_2}{R_2} \right) \frac{R_1 R_2}{R_1 + R_2}$$

$$= \frac{R_3}{\frac{R_1 R_3 + R_2 R_3 + R_1 R_2}{R_1 + R_2}} \cdot \frac{R_1 R_2}{R_1 + R_2} \left( \frac{E_1}{R_1} - \frac{E_2}{R_2} \right)$$

$$\frac{R_1 R_2 R_3}{R_1 R_3 + R_2 R_3 + R_1 R_2} \left( \frac{E_1}{R_1} - \frac{E_2}{R_2} \right) =$$

$$V_{AB} = \boxed{\frac{R_2 R_3 E_1 - R_1 R_3 E_2}{R_1 R_2 + R_2 R_3 + R_1 R_2}}$$

Notion