 


Sequential circuits Tutorial Session – 2


1. SR Latch:

The two inputs A and B are connected to a NOR based SR latch, via two AND gates as shown in the figure.
If $A = 1$ and $B = 1$, give the values of the output Q and \bar{Q} .



 2. SR Latch:

Plain S-R latch circuits are “set” by activating the S input and de-activating the R input. Conversely, they are “reset” by activating the R input and de-activating the S input. Gated latches and flip-flops, however, are a little more complex:



Describe what input conditions have to be present to force each of these multivibrator circuits to *set* and to *reset*.

For the S-R gated latch:



Set by ...
Reset by ...

For the S-R flip-flop:

Set by ...
Reset by ...

  3. SR Latch:


Determine the output states for this S-R flip-flop, given the pulse inputs shown:



 
4. Flip-Flop and Timing Diagrams:

Complete the timing diagram for the specified flip-flop such the output Q will be as indicated. Assume that the input signal can change only on the vertical lines. Also, assume that the setup time t_{su} and the hold time t_h are each equal to the width of one square.


a- Complete the timing diagram for the D input to a negative-edge triggered D flip-flop.



 b- Complete the timing diagram for the T input to a negative-edge triggered T flip-flop.





 c- Complete the timing diagram for the J input to a negative-edge triggered JK flip-flop.



  
5. D Latch:

Determine the final output states over time for the following circuit, built from D-type gated latches:
 At what specific times in the pulse diagram does the final output assume the input's state?
 How does this behavior differ from the normal response of a D-type latch?



 
6. Propagation delay of logic gates:

Usually, propagation delay is considered an undesirable characteristic of logic gates, which we simply have to live with. Other times, it is a useful, even necessary, trait. Take for example this circuit:





If the gates constituting this circuit had zero propagation delay, it would perform no useful function at all. To verify this sad fact, analyze its steady-state response to a "low" input signal, then to a "high" input signal. What state is the AND gate's output always in?

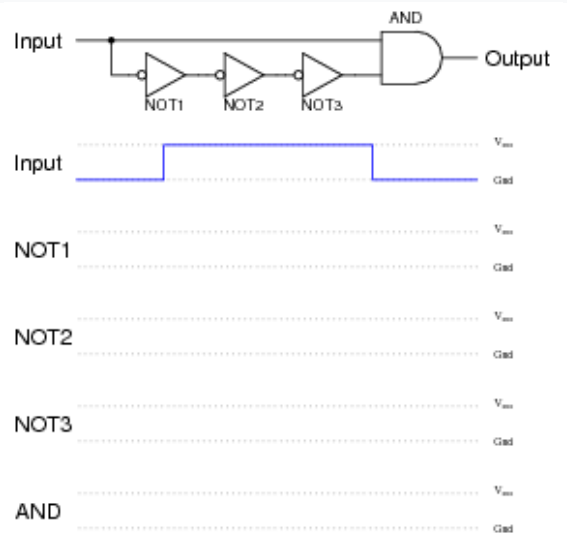Now, consider propagation delay in your analysis by completing a timing diagram for each gate's output, as the input signal transitions from low to high, then from high to low:



  
7. D Latch & Propagation delay of logic gates:

a- Determine the Q and Q output states of this D-type gated latch, given the following input conditions:



Determine the Q and Q output states of this D-type gated latch, given the following input conditions:

 
b- Now, suppose we add a propagation-delay-based one-shot circuit to the Enable line of this D-type gated latch. Re-analyze the output of the circuit, given the same input conditions:



Comment on the differences between these two circuits' responses, especially with reference to the enabling input signal (B).

 
8. D Latch:

Shown here are two digital components: a D-type *latch* and a D-type *flip-flop*:
 Other than the silly name, what distinguishes a “flip-flop” from a latch? How do the two circuits differ in function?




 
9. D flip-flop:

Determine the output states for this D flip-flop, given the pulse inputs shown:



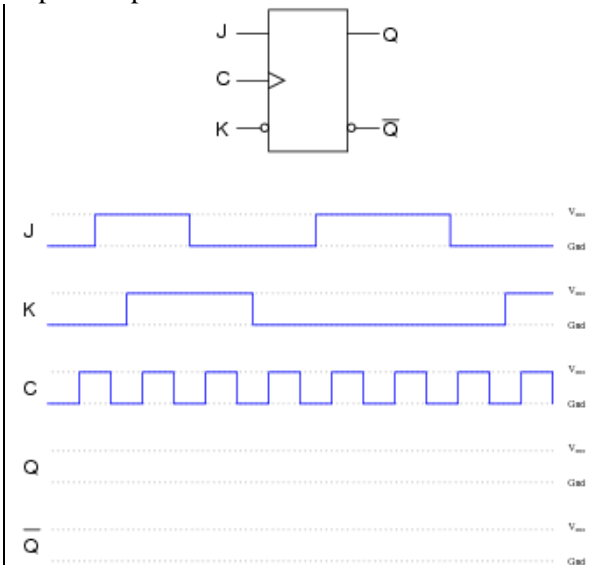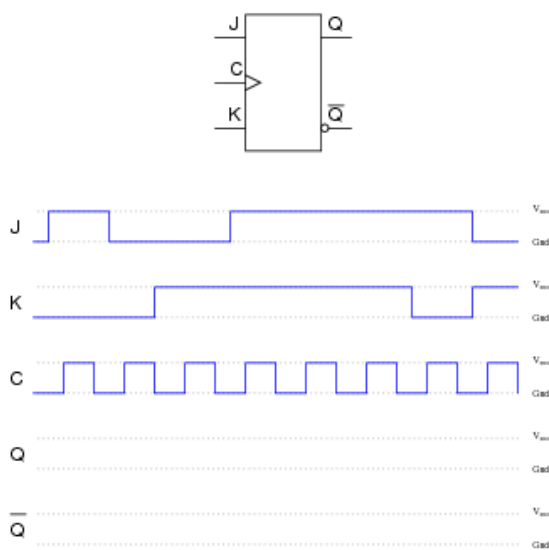
10. JK Flip-Flop:

Determine the output states for these J-K flip-flops, given the pulse inputs shown:



 
11. D flip-flop:

For the 74LS74 **D flip-flop** shown in the following figure, complete the timing diagram for the output signal **Q**. **Note** that the **CLK** input (clock) for this flip-flop is a positive edge **trigger** and both the **PR** and **CLR** asynchronous inputs (Preset and Clear) are active low.



 
12. JK Flip-Flop:

For the 74LS76 **JK flip-flop** shown in the following figure, complete the timing diagram for the output signal **Q**. **Note** that the **CLK** input for this flip-flop is a negative edge **trigger** and both the **PR** and **CLR** asynchronous inputs (Preset and Clear) are active low.



 
13. JK Flip-Flop as a divide-by-two circuit:

A divider-by-two circuit is implemented with a JK flip-flop. It generates a clock output that is half the frequency of the clock input. Predict the timing diagram for a **JK Divider-by-two** circuit.



 
14. D Flip-Flop:

For the sequential circuit below, draw the waveform of the output (Q_A).




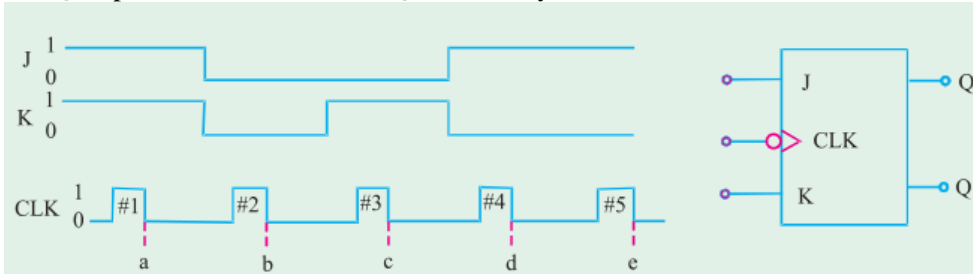15. JK Flip-Flop:

The following figure shows the waveforms applied at J, K and CLK inputs of the clocked J-K flip-flop. Sketch the Q output waveform. Assume $Q = 0$ initially.




 What will be the output waveform Q of a J-K flip-flop if the following waveforms are applied at the input? Assume the flip-flop triggers at the falling edge of clock pulse.



 
16. D Flip-Flop:

An edge-triggered D Flip-flop can be made to operate in the toggle mode by connecting it as shown below. Assume $Q = 0$ initially and determine the Q (output) waveform.



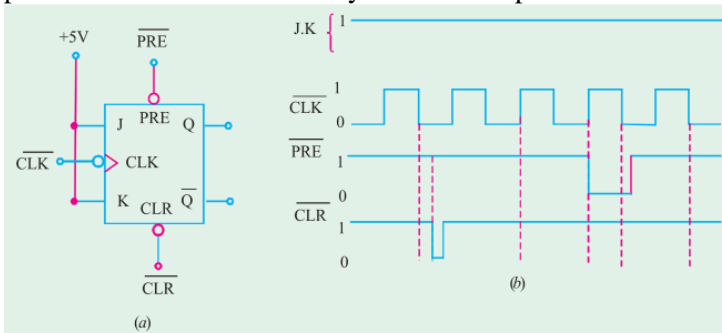17. Clocked J-K Flip-Flop with Asynchronous Inputs:

The following figure (a) shows the logic symbol for a J-K flip-flop that responds to the falling edge on its clock pulse and has active-LOW asynchronous inputs. The J and K inputs are tied HIGH.



Using the following true table, determine the Q-output in response to the waveforms shown in Fig. (b). Assume that initially $Q = 0$.

(a) Symbol

Inputs			Output Q
J	K	CLK	Q
0	0	↓	Q_0 (no change)
1	0	↓	1
0	1	↓	0
1	1	↓	Q_0 (toggles)

(b) Truth table

Fig. Falling edge triggered J-K flip-flop.

(a) Symbol

Inputs		Output / Flip-flop response
PRESET	CLEAR	
1	1	Clocked operation*
0	1	$Q = 1$ (regardless of CLK)
1	0	$Q = 0$ (regardless of CLK)
0	0	Not used

(b) Truth table