 


Sequential circuits Tutorial Session – 2 (with Answers)

1. SR Latch:

The two inputs A and B are connected to a NOR based SR latch, via two AND gates as shown in the figure. If $A = 1$ and $B = 1$, give the values of the output Q and \bar{Q} .



Answer 1:

From the given diagram,

$$S = A\bar{Q}, R = QB$$

Given that, $A = 1, B = 0$

$$S = \bar{Q}, R = 0$$

The truth table of the S-R latch is:

S	R	Q_{n+1}
0	0	No Change
0	1	0
1	0	1
1	1	Invalid state

Let $Q = 0$,

$$S = \bar{Q} = 1, R = 0 \Rightarrow Q_{n+1} = 1$$

Let $Q = 1$,


$$S = \bar{Q} = 0, R = 0 \Rightarrow Q_{n+1} = 1$$

In both the cases, $Q_{n+1}\bar{Q}_{n+1} = 10$


2. SR Latch:

Plain S-R latch circuits are “set” by activating the S input and de-activating the R input. Conversely, they are “reset” by activating the R input and de-activating the S input. Gated latches and flip-flops, however, are a little more complex:

S-R gated latch

 

S-R flip-flop

 

Describe what input conditions have to be present to force each of these multivibrator circuits to *set* and to *reset*.

For the S-R gated latch:

Set by ...
Reset by ...

For the S-R flip-flop:

Set by ...
Reset by ...

Answer 2:

For the S-R gated latch:



Set by making S high, R low, and E high.
Reset by making R high, S low, and E high.

For the S-R flip-flop:


Set by making S high, R low, and C transition from low to high.
Reset by making R high, S low, and C transition from low to high.

3. SR Latch:

Determine the output states for this S-R flip-flop, given the pulse inputs shown:

  


Answer 3:

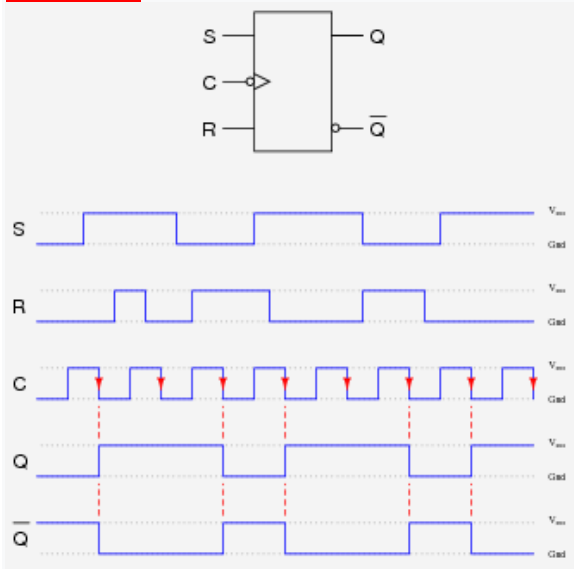

 
4. Flip-Flop and Timing Diagrams:

Complete the timing diagram for the specified flip-flop such the output Q will be as indicated. Assume that the input signal can change only on the vertical lines. Also, assume that the setup time t_{su} and the hold time t_h are each equal to the width of one square.


a- Complete the timing diagram for the D input to a negative-edge triggered D flip-flop.





 
b- Complete the timing diagram for the T input to a negative-edge triggered T flip-flop.



c- Complete the timing diagram for the J input to a negative-edge triggered JK flip-flop.

 

Answer 4:

  
 


5. D Latch:

Determine the final output states over time for the following circuit, built from D-type gated latches:

At what specific times in the pulse diagram does the final output assume the input's state?

How does this behavior differ from the normal response of a D-type latch?

  


Answer 5:

The final output assumes the same logic state as the input only when the enable input signal (B) *transitions* from “high” to “low”.


Notes:

 Note that by adding another latch, the overall behavior only slightly resembles the behavior of a D-type latch. With the addition of the second latch, we've changed this circuit into a *flip-flop*, specifically of the *master-slave* variety.



 
6. Propagation delay of logic gates:

Usually, propagation delay is considered an undesirable characteristic of logic gates, which we simply have to live with. Other times, it is a useful, even necessary, trait. Take for example this circuit:




If the gates constituting this circuit had zero propagation delay, it would perform no useful function at all. To verify this sad fact, analyze its steady-state response to a “low” input signal, then to a “high” input signal. What state is the AND gate's output always in?

Now, consider propagation delay in your analysis by completing a timing diagram for each gate's output, as the input signal transitions from low to high, then from high to low:

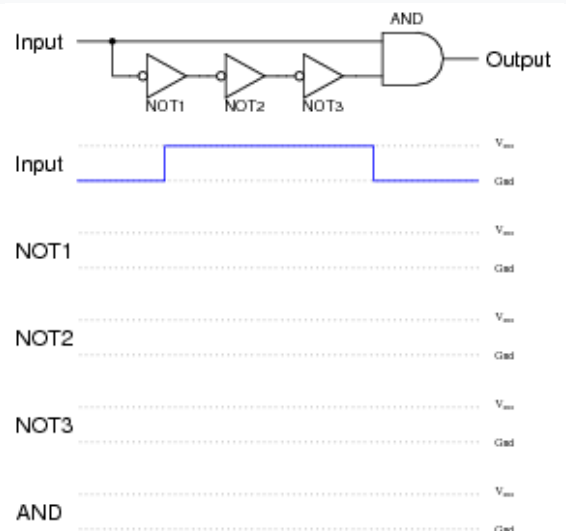


Answer 6:

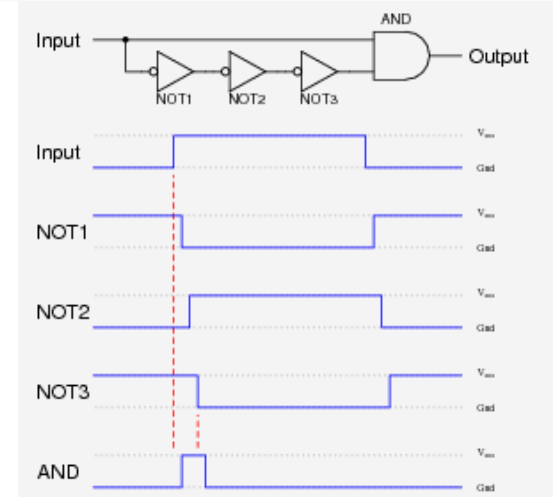Follow-up question: describe exactly what conditions are necessary to obtain a “high” signal from the output of this circuit, and what determines the duration of this “high” pulse. This circuit is a special type of *one-shot*, outputting a single pulse of limited duration for each leading-edge transition of the input signal.



 
7. D Latch & Propagation delay of logic gates:

a- Determine the Q and \bar{Q} output states of this D-type gated latch, given the following input conditions:




Determine the Q and \bar{Q} output states of this D-type gated latch, given the following input conditions:

Answer 7:

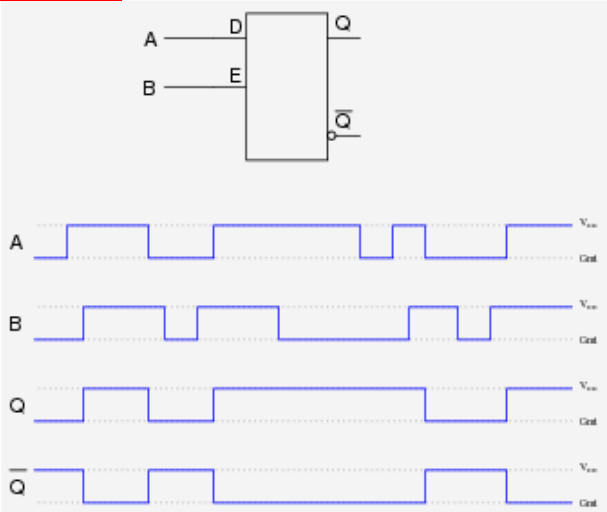

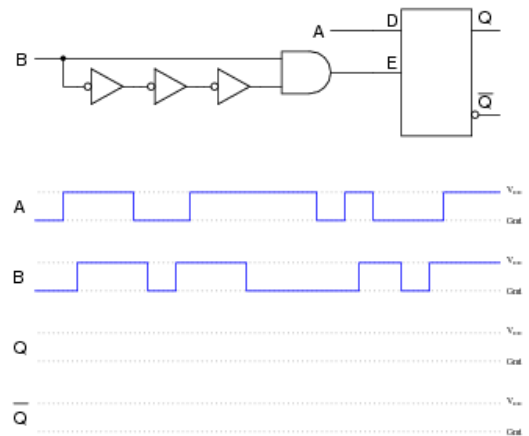b- Now, suppose we add a propagation-delay-based one-shot circuit to the Enable line of this D-type gated latch. Re-analyze the output of the circuit, given the same input conditions:



Comment on the differences between these two circuits' responses, especially with reference to the enabling input signal (B).


Follow-up question: one of these circuits is referred to as *edge-triggered*. Which one is it?

Challenge question: in reality, the output waveforms for both these scenarios will be shifted slightly due to propagation delays within the constituent gates. Re-draw the true outputs, accounting for these delays.

8. D Latch:

Shown here are two digital components: a D-type *latch* and a D-type *flip-flop*:

Other than the silly name, what distinguishes a "flip-flop" from a latch? How do the two circuits differ in function?

 


Answer 8:


A "flip-flop" is a latch that changes output only at the rising or falling *edge* of the clock pulse.

9. D flip-flop:

Determine the output states for this D flip-flop, given the pulse inputs shown:


 


Answer 9:


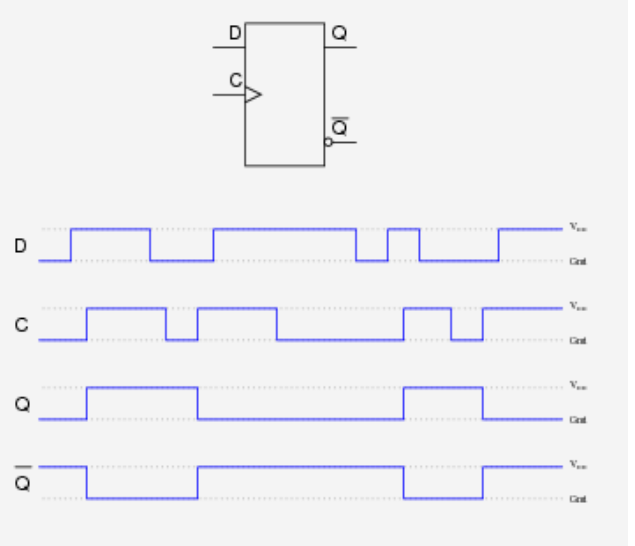


10. JK Flip-Flop:

Determine the output states for these J-K flip-flops, given the pulse inputs shown:

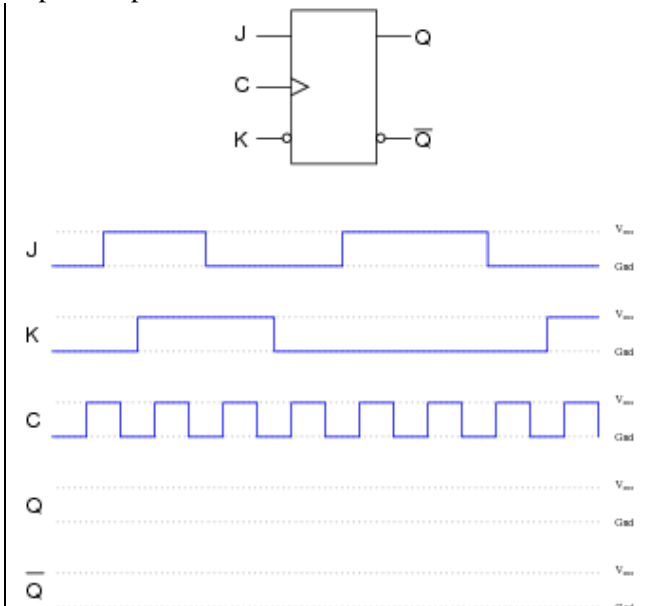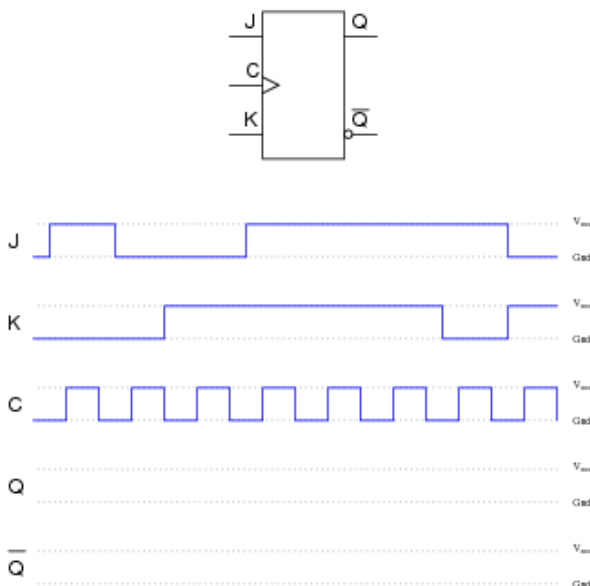


Answer 10:

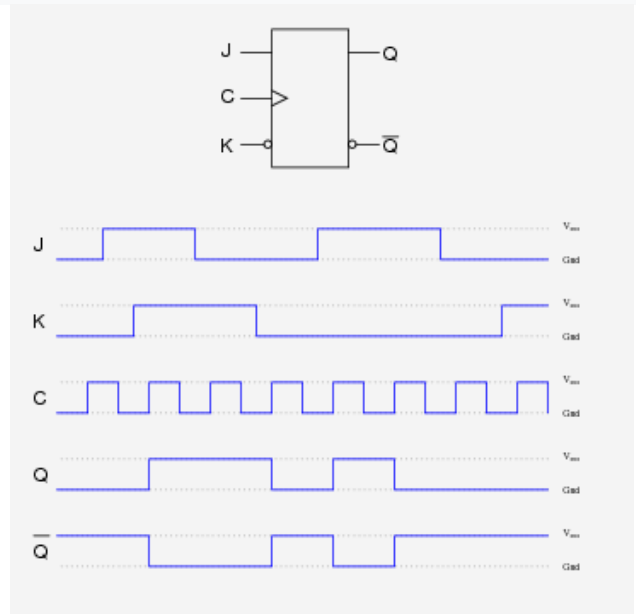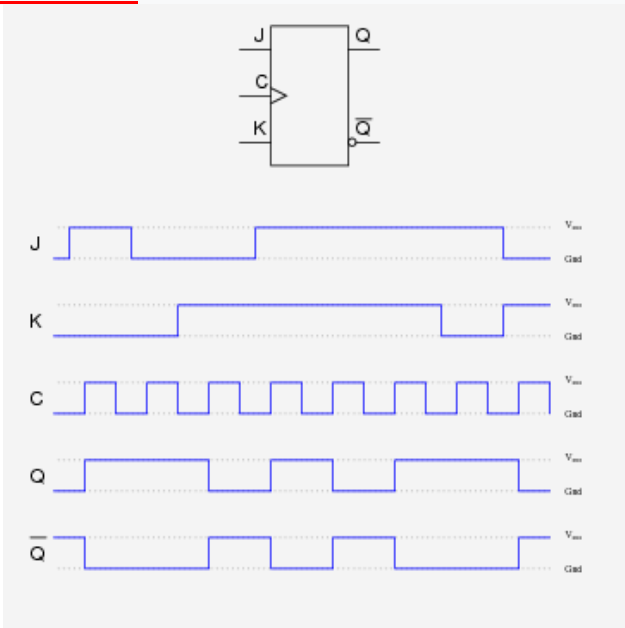


11. D flip-flop:

For the 74LS74 **D flip-flop** shown in the following figure, complete the timing diagram for the output signal **Q**. **Note** that the **CLK** input (clock) for this flip-flop is a positive edge **trigger** and both the **PR** and **CLR** asynchronous inputs (Preset and Clear) are active low.

 


Answer 11:

 


12. JK Flip-Flop:

For the 74LS76 **JK flip-flop** shown in the following figure, complete the timing diagram for the output signal **Q**. **Note** that the **CLK** input for this flip-flop is a negative edge **trigger** and both the **PR** and **CLR** asynchronous inputs (Preset and Clear) are active low.

 



Answer 12:

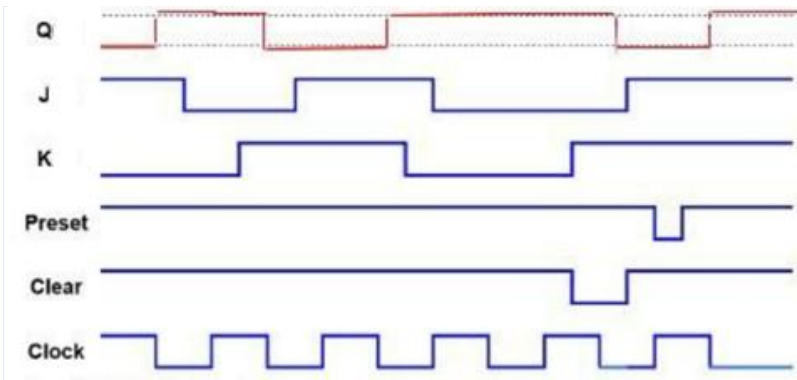

13. JK Flip-Flop as a divide-by-two circuit:



A divider-by-two circuit is implemented with a JK flip-flop. It generates a clock output that is half the frequency of the clock input. Predict the timing diagram for a **JK Divider-by-two circuit**.

Answer 13:

  


14. D Flip-Flop:

For the sequential circuit below, draw the waveform of the output (Q_A).

  


Answer 14:

 


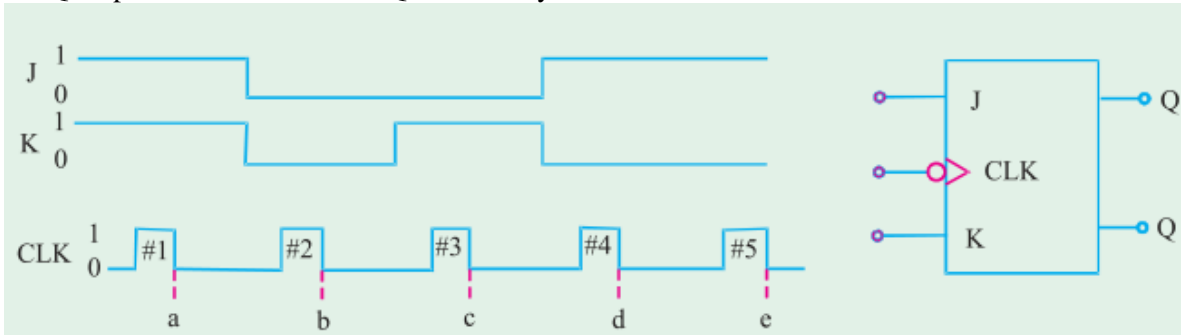15. JK Flip-Flop:

The following figure shows the waveforms applied at J, K and CLK inputs of the clocked J-K flip-flop. Sketch the Q output waveform Assume Q = 0 initially.



What will be the output waveform Q of a J-K flip-flop if the following waveforms are applied at the input? Assume the flip-flop triggers at the falling edge of clock pulse.

 

Answer 15:

Using the truth table of clocked J-K flip-flop, the waveforms the Q-waveform sketch is:



 


Fig. Falling edge triggered J-K flip-flop.

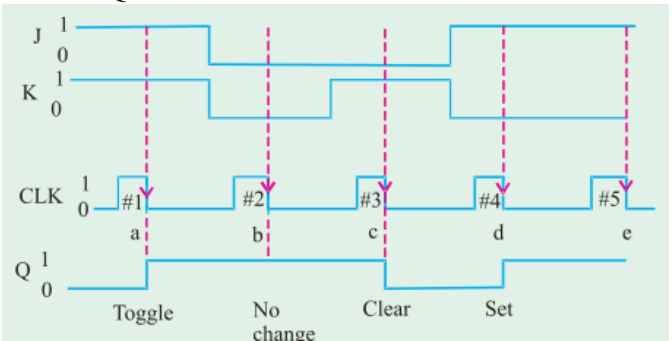

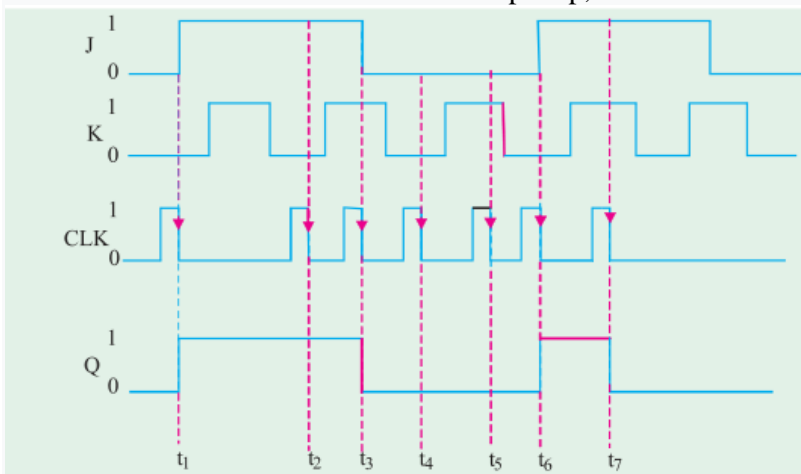
Recall the truth table of a clocked J-K flip-flop, We can sketch the Q-output waveform as shown in Fig:



16. D Flip-Flop:


An edge-triggered D Flip-flop can be made to operate in the toggle mode by connecting it as shown below.

Assume Q = 0 initially and determine the Q (output) waveform.

 


Answer 16:

 The clock is 1 kHz waveform. The output waveform can be obtained from the input as shown in Fig.



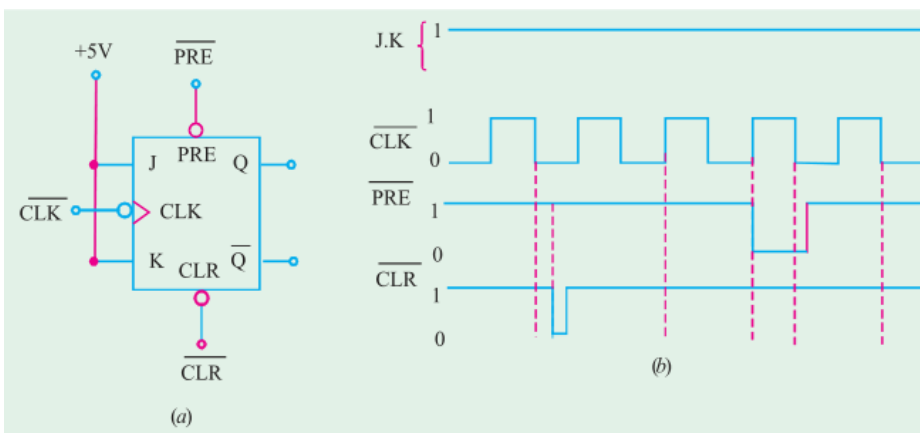17. Clocked J-K Flip-Flop with Asynchronous Inputs:

The following figure shows the logic symbol for a J-K flip-flop that responds to the falling edge on its clock pulse and has active-LOW asynchronous inputs. The J and K inputs are tied HIGH.



Using the following true tables, determine the Q-output in response to the waveforms shown in Fig. (b). Assume that initially Q = 0.


 


Fig. Falling edge triggered J-K flip-flop.

 

(b) Truth table

Answer 17:

In order to sketch the Q-output waveform, recall the truth tables of J-K flip-flop

